

High frequency effects in inverter-fed AC electric machinery

Andreas Binder

**Darmstadt University of Technology
Institute for Electrical Energy Conversion
abinder@ew.tu-darmstadt.de**



TECHNISCHE UNIVERSITÄT DARMSTADT
Institute for Electrical Energy Conversion



Prof. A. Binder
1



Fast voltage change rates du/dt

- Fast switching IGBT inverters: short **voltage rise time** t_r between zero and DC link voltage 100 ns:


$$du / dt \cong U_d / t_r$$

<i>Line supply</i>	<i>dc link voltage</i>	$du / dt \cong U_d / t_r$
Single phase 230 V 50 Hz	310 V	3.1 kV/ μ s
Three phase 400 V 50 Hz	560 V	5.6 kV/ μ s
Three phase 500 V 50 Hz	700 V	7.0 kV/ μ s

- “Steep voltage pulses” means, that the wave propagation time between inverter and motor on the motor cable is in THE SAME ORDER OF MAGNITUDE as the time for voltage build up.
- So wave propagation effects (= wave reflection) become significant!**



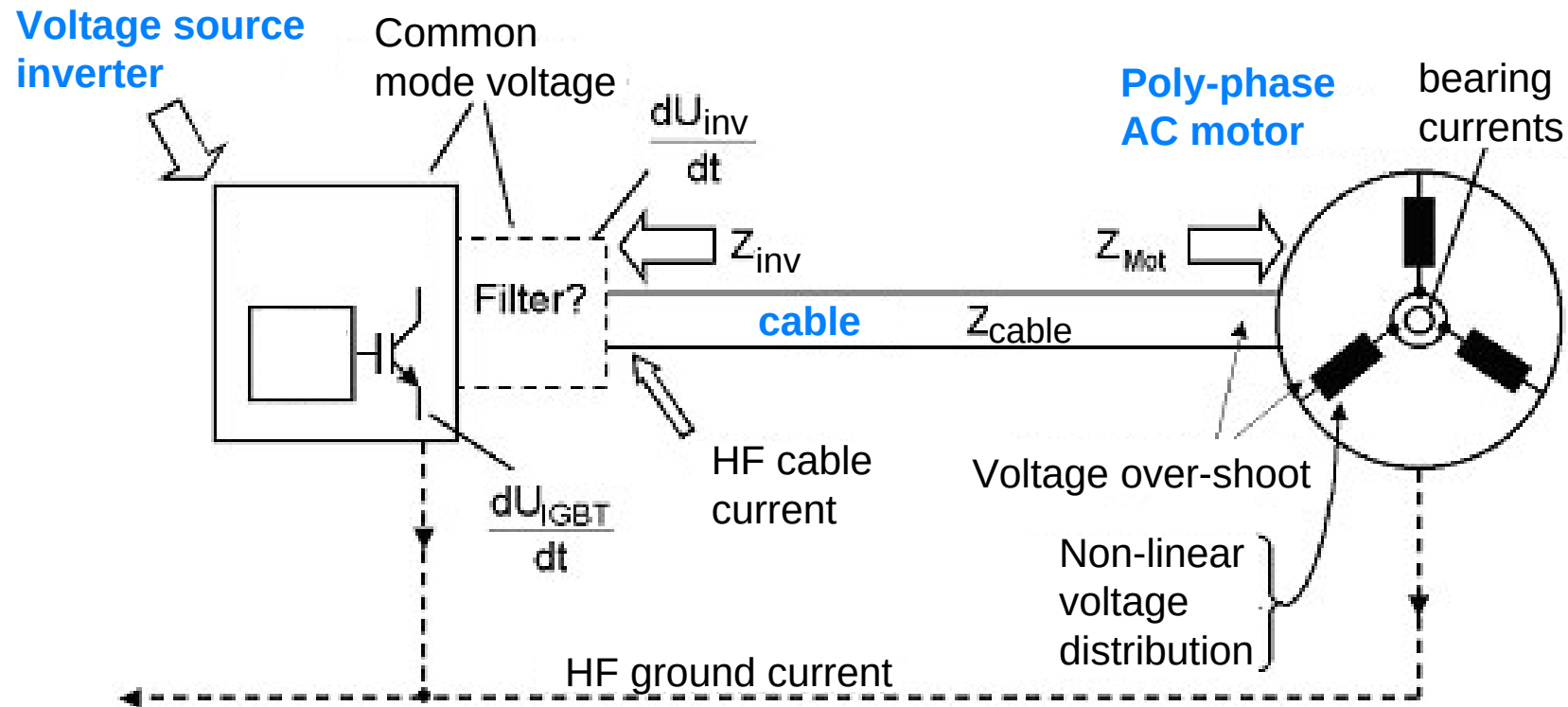Inverter-fed electrical machines as drive system



Source: DFG research group FOR575:
Binder/Mutschler, TU Darmstadt



High frequency effects in inverter-fed AC electric machinery

High du/dt = steep inverter voltage front:

- Voltage overshoot at motor winding terminals
- Non-linear voltage distribution per phase leads to voltage stress

HF common mode inverter output voltage:

- HF ground currents via motor main insulation
- Cable loading due to HF capacitive cable current
- HF parasitic bearing currents
- HF electromagnetic interference via cable and radiation



High frequency effects in inverter-fed AC electric machinery

- 1 Voltage wave reflections at motor terminals
- 2 HF voltage distribution in armature winding
- 3 Insulation stress of AC winding at inverter supply
- 4 Parasitic HF currents
- 5 System design of inverter drives coping with big du/dt




Voltage wave reflection at motor terminals

Wave propagation velocity v

Permittivity & permeability of medium:
 ϵ, μ

Voltage wave amplitude: u

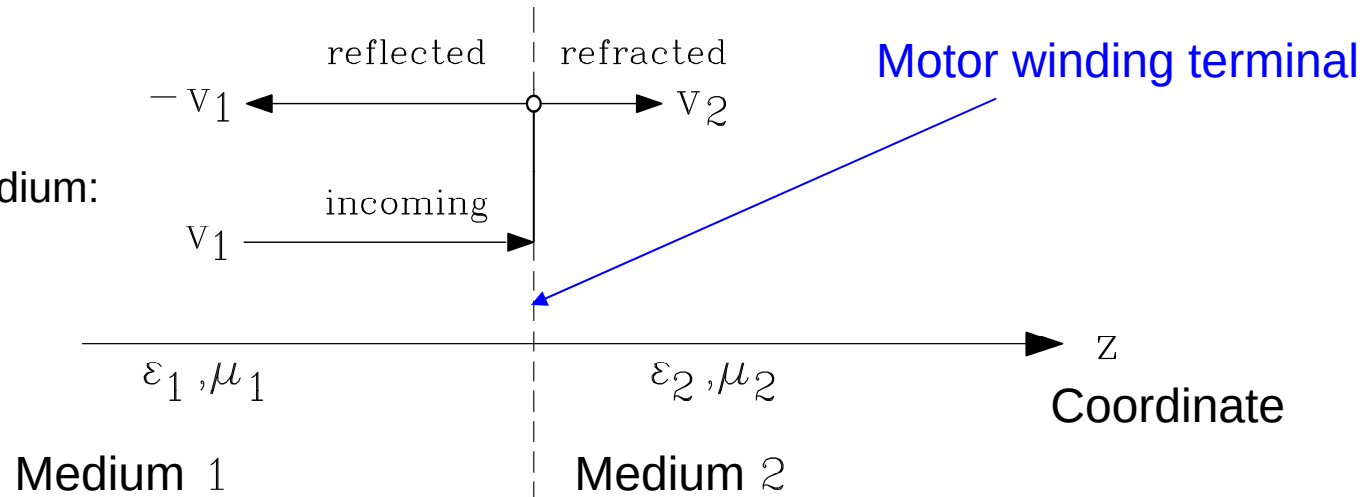

1: Motor cable:

low wave impedance Z_{cable}

2: Motor winding:

high wave impedance Z_{mot}

$$\frac{u_{\text{reflected}}}{u_{\text{incom}}} = r = \frac{Z - Z_{\text{cable}}}{Z + Z_{\text{cable}}}$$



Voltage wave reflection coefficient r

$$\frac{u_{\text{reflected}}}{u_{\text{incom}}} = r = \frac{Z - Z_{\text{cable}}}{Z + Z_{\text{cable}}}$$


Positive voltage wave reflection at motor terminals: voltage increased

$$r_{\text{mot}} = \frac{Z_{\text{mot}} - Z_{\text{cable}}}{Z_{\text{mot}} + Z_{\text{cable}}} \quad Z_{\text{mot}} \rightarrow \infty : \quad r_{\text{mot}} = 1$$

Negative voltage wave reflection at inverter, because DC link capacitor is HF short circuit
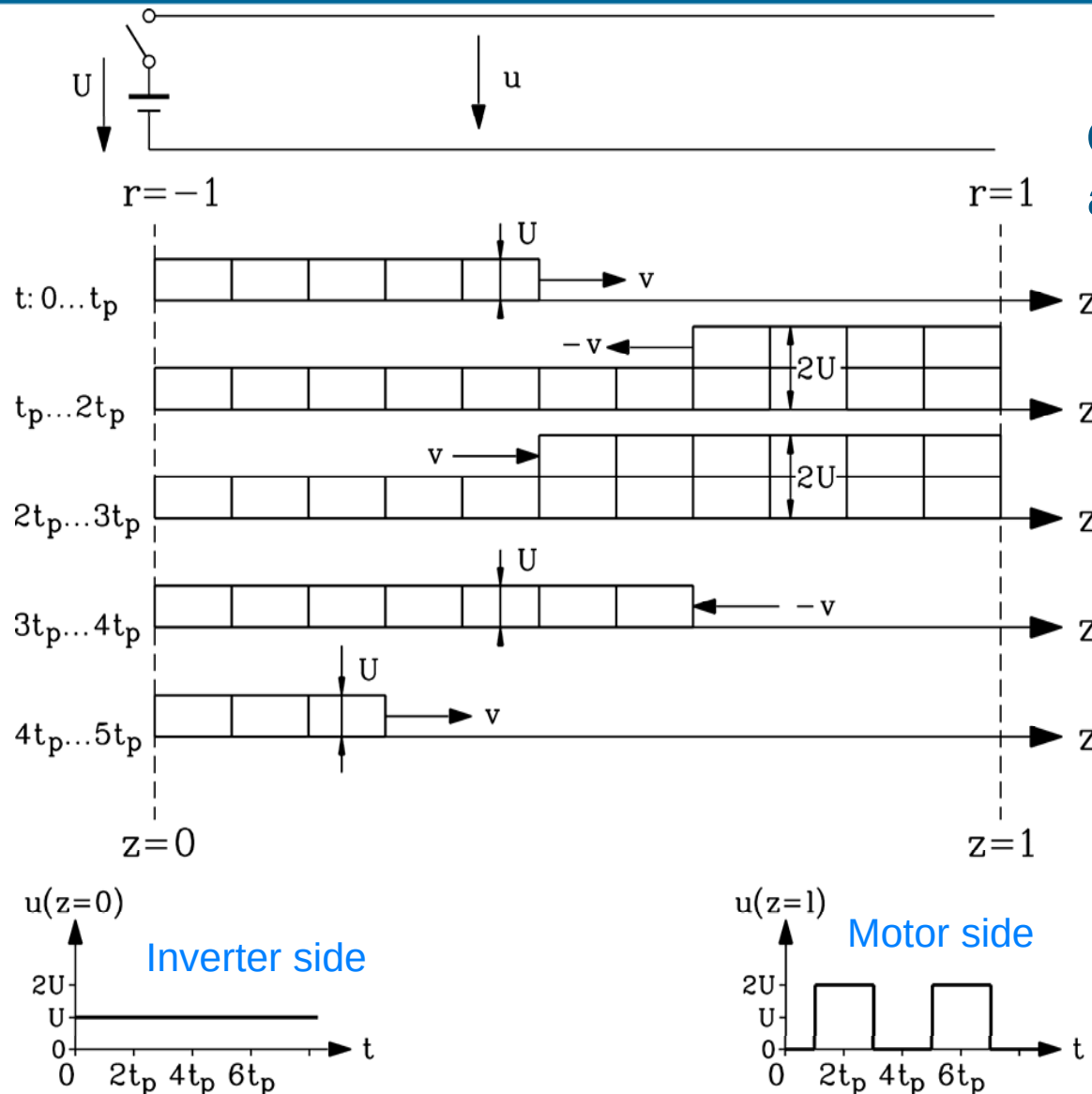
$$r_{\text{inv}} = \frac{Z_{\text{inv}} - Z_{\text{cable}}}{Z_{\text{inv}} + Z_{\text{cable}}} \quad Z_{\text{inv}} \rightarrow 0 : \quad r_{\text{inv}} = -1$$





Oscillation of voltage at motor terminal

- Motor side: "Open cable end": $Z_{\text{mot}} \rightarrow \infty$, $r_{\text{mot}} = 1$
- Inverter: "Short-circuited cable end": $Z_{\text{inv}} = 0$, $r_{\text{inv}} = -1$

Wave reflection at both ends of cable:

- a) Motor side:
Voltage oscillation with twice dc link voltage
- b) Inverter side:
No oscillation



Simple single phase motor cable

Example:

PVC-insulated cable H05VVF4G1.5: $4 \times 1.5 \text{ mm}^2$


conductor diameter $d = 1.4 \text{ mm}$, $q = d^2 \pi / 4 = 1.5 \text{ mm}^2$

cable length $l_c = 100 \text{ m}$

distance between conductor centres: $a = 4.15 \text{ mm}$,

average relative permittivity: $\epsilon_r = 4$

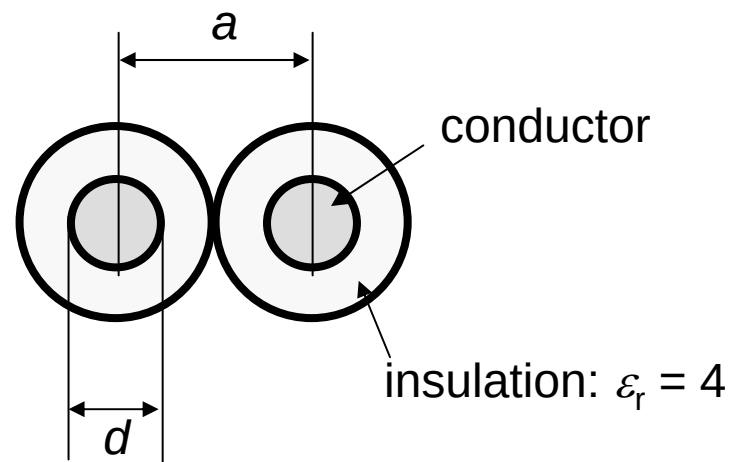HF current flows on conductor surface, so no inner inductance occurs!



Motor cable parameters

Phase outer inductance per unit length: $L'_{\text{cable}} = \frac{\mu_0}{2\pi} \cdot \ln\left(\frac{2a}{d}\right) = 0.36 \mu\text{H/m}$

Phase capacitance per unit length: $C'_{\text{cable}} = 2\pi \cdot \varepsilon_r \cdot \varepsilon_0 / \ln(2a / d) = 125 \text{ pF/m}$

Cable wave impedance ($R' \approx 0, G' \approx 0$): $Z_{\text{cable}} = \sqrt{\frac{L'_{\text{cable}}}{C'_{\text{cable}}}} = \underline{\underline{53.7 \Omega}}$ measured: 83Ω

Wave velocity : $v = \frac{1}{\sqrt{L'_{\text{cable}} C'_{\text{cable}}}} = \underline{\underline{149 \cdot 10^6 \text{ m/s}}} \approx 150\,000 \text{ km/s}$

$$v \cong \frac{c_0}{2} = 150\,000 \text{ km/s}$$



Motor cable voltage reflection

DC link voltage 560 V, motor reflection coefficient (“worst case”):

$$r_{\text{mot}} = 1$$

Line to line over-voltage at motor terminals:


$$\hat{U}_{\text{LL,mot}} = (1 + r_{\text{mot}}) \cdot U_{\text{d}} = 2 \cdot 560 = \underline{\underline{1120 \text{ V}}}$$

Wave propagation time: $t_{\text{p}} = l_{\text{c}} / v = 100 / (150 \cdot 10^6) = 0.67 \mu\text{s}$

$$1/(4t_{\text{p}}) = \mathbf{375 \text{ kHz}}$$



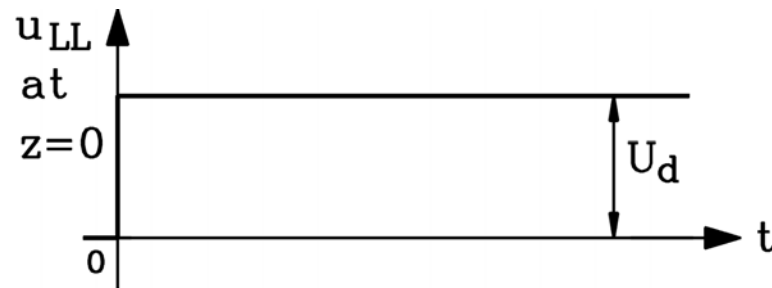
Motor reflection coefficient $r_{\text{mot}} = 0.75 < 1$



inverter side

Assumption:

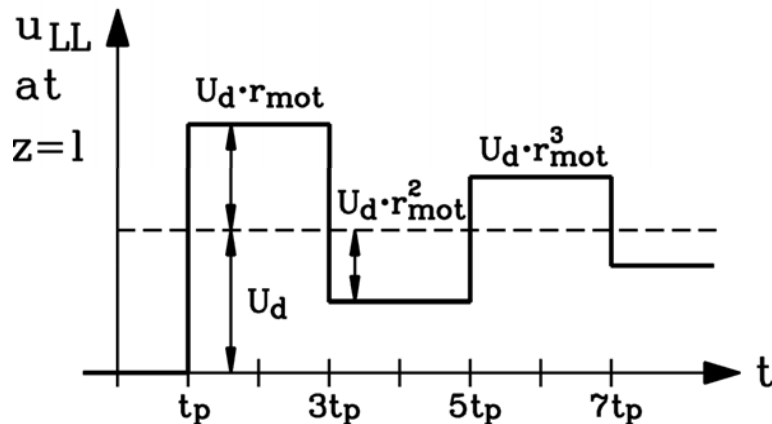Voltage rise time $t_r = 0$,
 $du/dt \rightarrow \infty$



motor side
 $r_{\text{mot}} = 0.75$

Oscillation of voltage at motor side end due to wave reflection at both ends of loss-free-cable:

Reflection coefficient: $r_{\text{mot}} = 0.75$ on motor side
 $r_{\text{inv}} = -1$ at inverter side.



Influence of motor size on cable and motor wave impedance

Wave impedance of motor cables Z_{cable} is more or less independent from rated cable current!

Motor impedance is determined by $Z_{\text{mot}} = 2\pi \cdot f \cdot \sigma \cdot L_s$

Frequency f

Total motor flux leakage coefficient σ

Stator motor inductance per phase $L_s \sim (N_s)^2$

Number of turns per phase N_s

At a given rated voltage U_N the number of turns per phase N_s decreases with motor size.

Motor impedance Z_{mot} **decreases** with increased motor size!



Influence of motor size on reflection coefficient

Example:

Four pole induction motor 400 V, 50 Hz

a) Small 1.1 kW-motor:

2.1 A, frame size 90 mm, measured motor wave impedance $Z_{\text{mot}} = 5000 \text{ Ohm}$.
Motor cable 4 x 1.5 mm², Type H05VVF4G1.5: current density: 1.4 A/mm²,
Cable wave impedance $Z_{\text{mot}} = 83 \text{ Ohm}$,

Motor reflection coefficient:
$$r_{\text{mot}} = \frac{5000 - 83}{5000 + 83} = \underline{\underline{0.967}}$$



b) Bigger 18.5 kW-motor:

frame size 180 mm, wave impedance 570 Ohm.
Motor cable wave impedance 75 Ohm.

Motor reflection coefficient:
$$r_{\text{mot}} = \frac{570 - 75}{570 + 75} = \underline{\underline{0.77}}$$



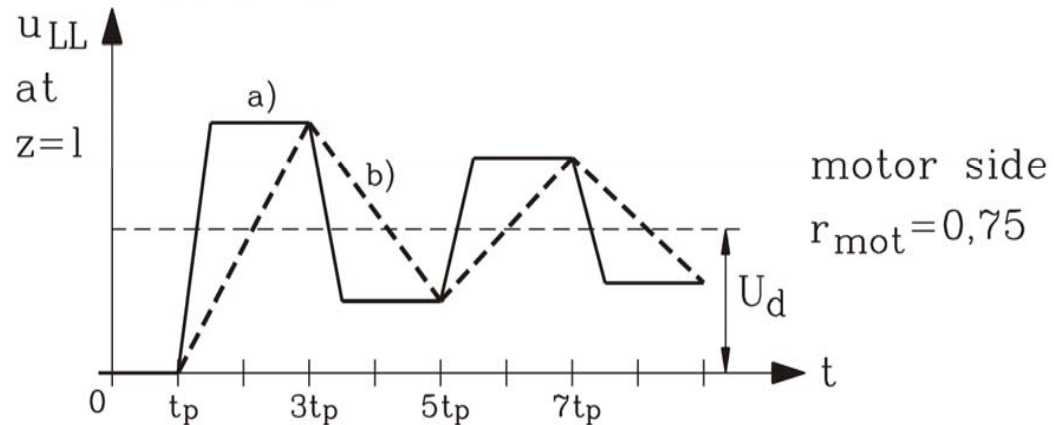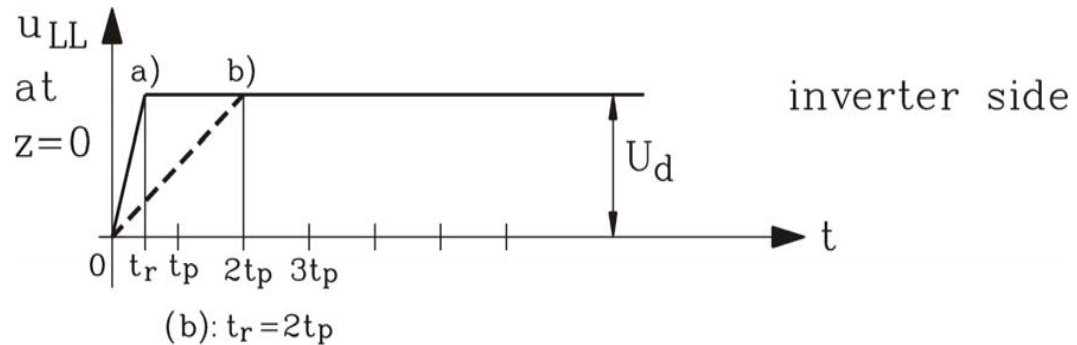Critical cable length $l_{c,crit}$ at $du/dt \cong U_d / t_r$



- For a given voltage rise time t_r of the inverter, a **"critical cable length"** $l_{c,crit}$ exists, where $t_r = 2t_p$.

- Longer cables lead to full voltage overshoot, as $t_r < 2t_p$!

- Shorter cables lead to reduced voltage overshoot: as $t_r > 2t_p$.

$$t_r = 2t_p = 2 \cdot l_c / v \Rightarrow l_{c,crit} = v \cdot t_r / 2$$



Example: Critical cable length $l_{c,crit}$

$$t_r = 2t_p = 2 \cdot l_c / v \Rightarrow l_{c,crit} = v \cdot t_r / 2$$


Voltage rise time $t_r = 100 \text{ ns}$,

Voltage wave propagation velocity $v = c_0/2 = 150\,000 \text{ km/s}$

$$l_{c,crit} = v \cdot t_r / 2 = 150 \cdot 10^6 \cdot 100 \cdot 10^{-9} / 2 = 7.5 \text{ m}$$

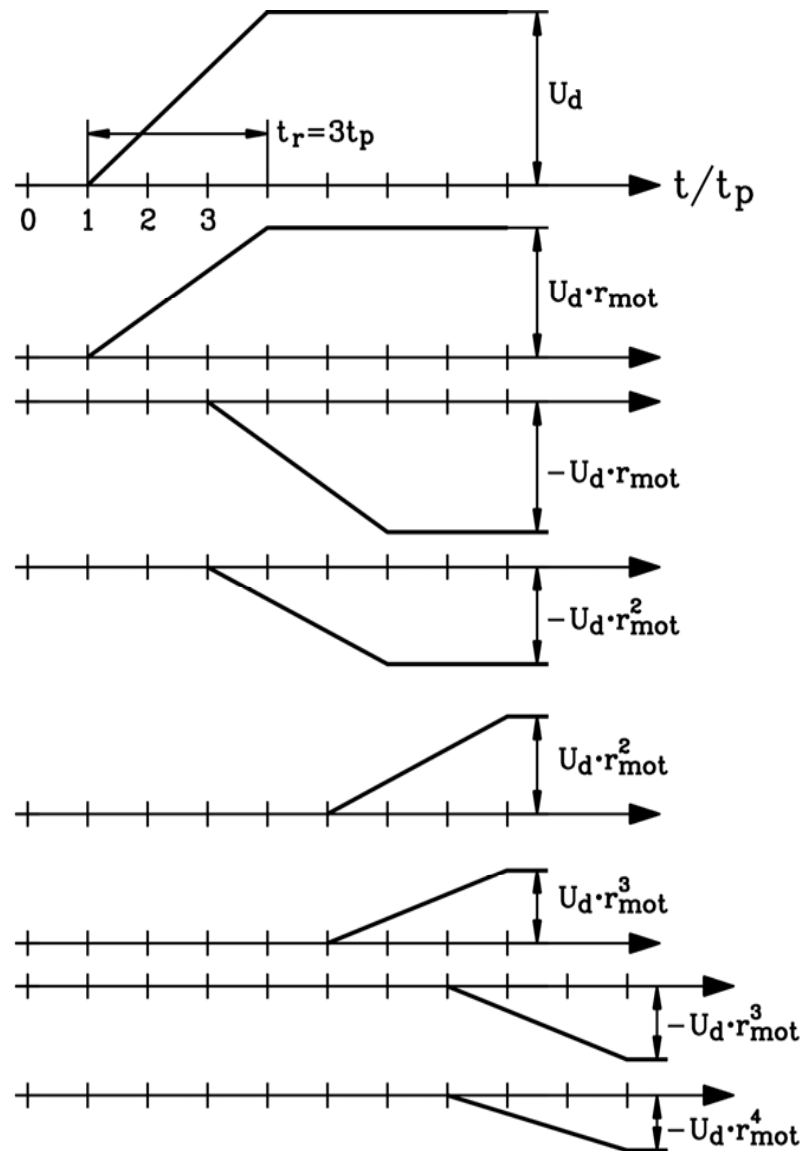If the cable is longer than 7.5 m between inverter and motor, then full voltage wave reflection occurs at the motor terminals!






Voltage reflection at short cable length $l < l_{c,crit}$


- Oscillating voltage overshoot at motor side due to wave reflection
- Does not reach its worst-case maximum value $(1+r_{mot})U_d = 1.75U_d$, but only $1.3U_d$, as $t_r > 2t_p$!

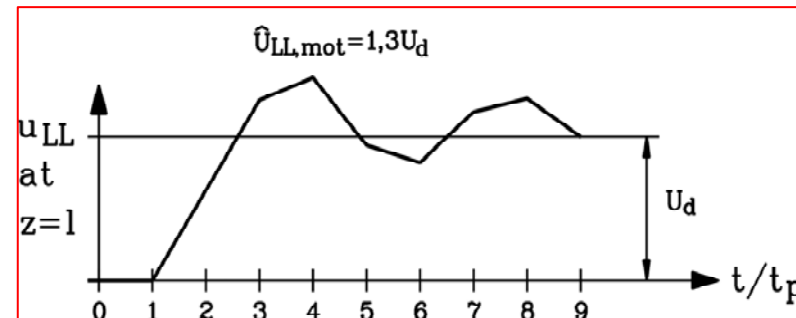Example:

- Motor reflection coefficient $r_{mot} = 0.75$
- Inverter reflection coefficient $r_{inv} = -1$
- Voltage rise time $t_r = 3t_p$



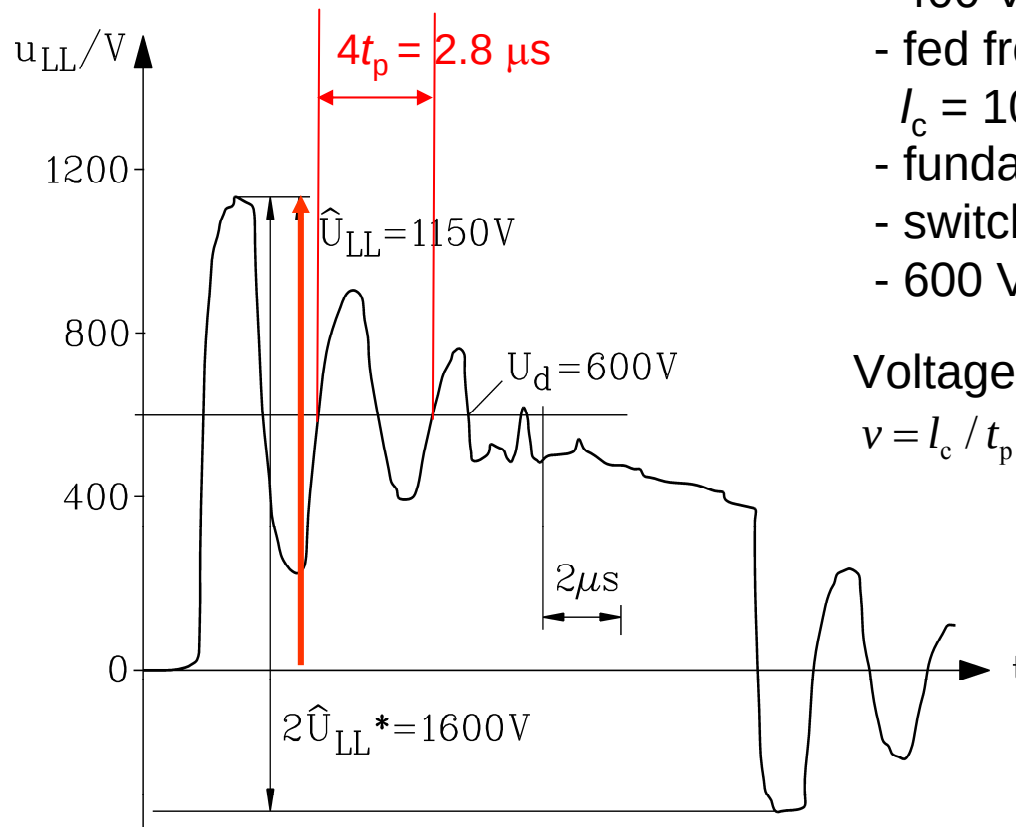Measured voltage reflection at long cable $l > l_{c,crit}$



Source: Siemens AG

- 2 pole induction motor, frame size 80 mm, 400 V, Y,
- fed from IGBT-inverter with motor cable $l_c = 100$ m,
- fundamental frequency $f_s = 30$ Hz
- switching frequency $f_T = 8$ kHz
- 600 V DC link voltage


Voltage wave velocity along the cable:

$$v = l_c / t_p = (100 \cdot 4 / 2.8) \cdot 10^6 = 143000 \text{ km/s} = 0.48c_0$$

Voltage reflection coefficient:


$$r_{mot} = (1150 - 600) / 600 = 0.92$$



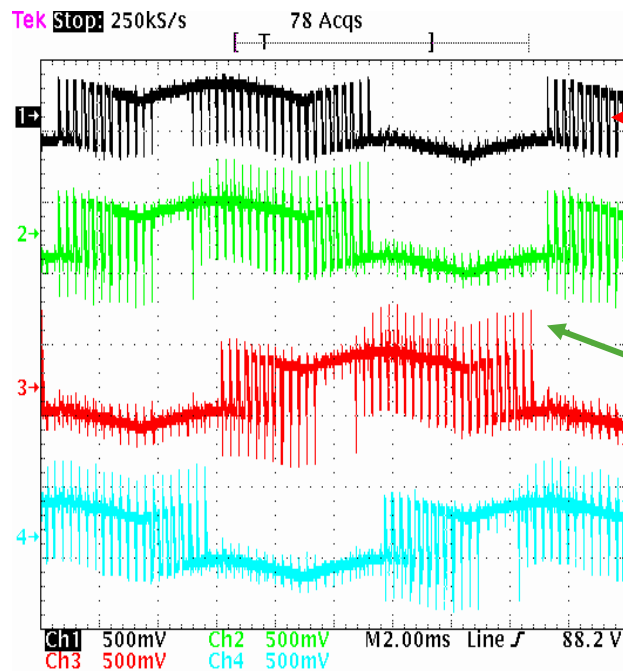

Measured voltage reflection at long cable

$I > I_{c,crit}$

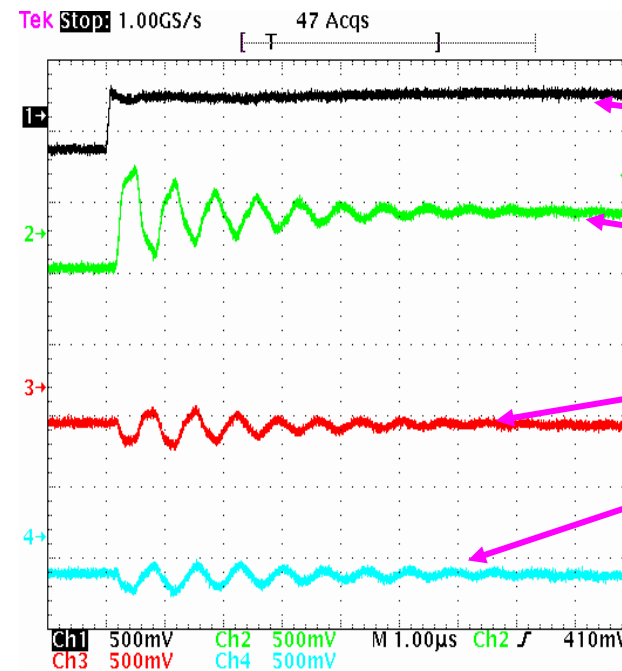

Source: Siemens AG



High frequency effects in inverter-fed AC electric machinery

Summary: Voltage wave reflections at motor terminals

- Fast IGBT switching yields high du/dt
- Large motor impedance vs. small cable impedance yields voltage reflections
- Fast switching leads to low critical cable length, where big reflections occur
- Fast switching causes increased voltage insulation stress of winding




High frequency effects in inverter-fed AC electric machinery

- 1 Voltage wave reflections at motor terminals
- 2 HF voltage distribution in armature winding
- 3 Insulation stress of AC winding at inverter supply
- 4 Parasitic HF currents
- 5 System design of inverter drives coping with big du/dt




HF voltage distribution in armature winding

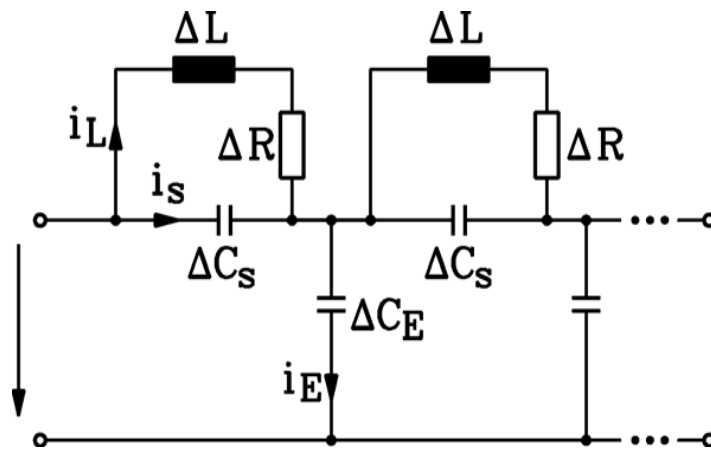- HF equivalent circuit for armature winding per phase
- *Kirchhoff's* laws applied to one element of equivalent circuit



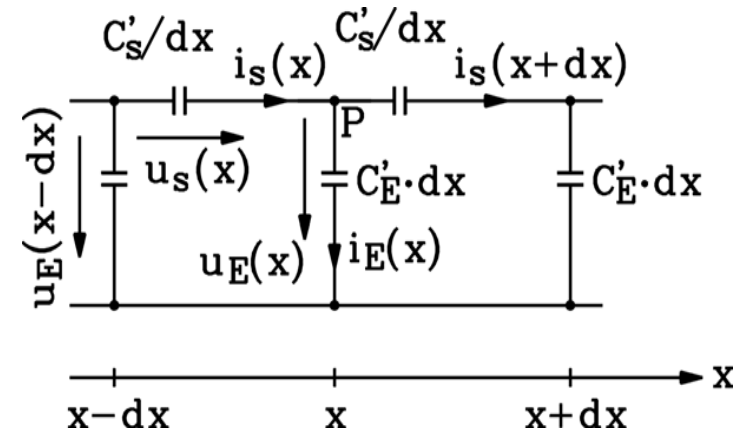Source: Heller-Veverka, VEB-Verlag Technik, Berlin, 1957



Motor winding equivalent circuit per turn consists of


- inductance per turn ΔL ,
- line-to-earth capacitance ΔC_E between conductor and stator iron,
- series capacitance ΔC_s between conductors of adjacent turns in slot.

Ground current: $\int i_E(x) \cdot dx / l = i_g$

For HF the inductance gives an “infinite” impedance!



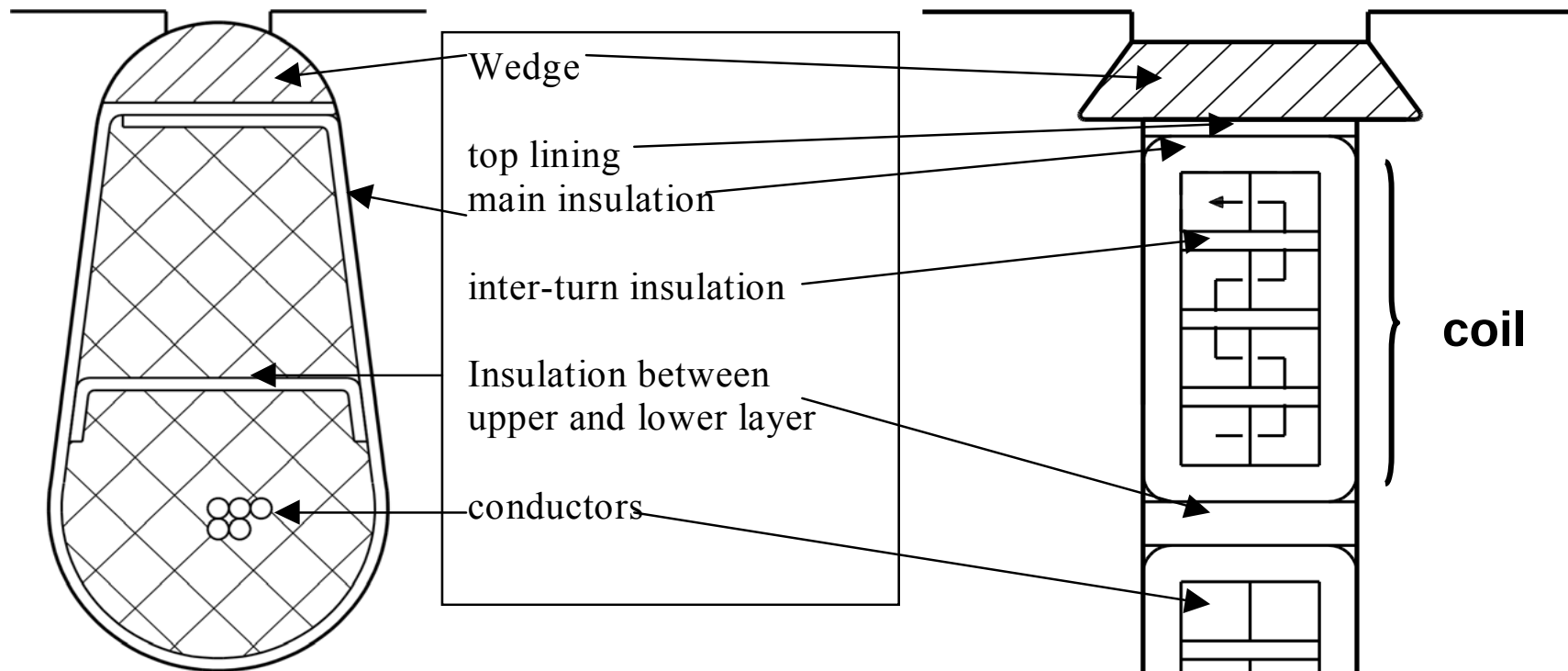Example: Two-layer motor winding: Slot and coil insulation



Oval semi-closed slot for round wire low voltage

Rectangular slot for form wound high voltage coil arrangement with $N_c = 8$ turns per coil



Capacities in the stator winding

- N_s turns per winding
- Length of winding per turn: Δx ,
- winding length $l = \Delta x \cdot N_s$
- Total **line-to-earth** capacitance
- Total **series** capacitance per phase

$$C_E = N_s \cdot \Delta C_E$$

$$C_s = \Delta C_s / N_s$$

$$\Delta C_E = C_E / N_s = (C_E / l) \cdot \Delta x = C_E' \cdot \Delta x$$


$$\Delta C_s = C_s \cdot N_s = C_s \cdot l / \Delta x = C_s' / \Delta x$$



for Fig.: $\Delta C_E < \Delta C_s$

Per turn:
series capacitance ΔC_s

Per turn:
line-to-earth capacitance ΔC_E

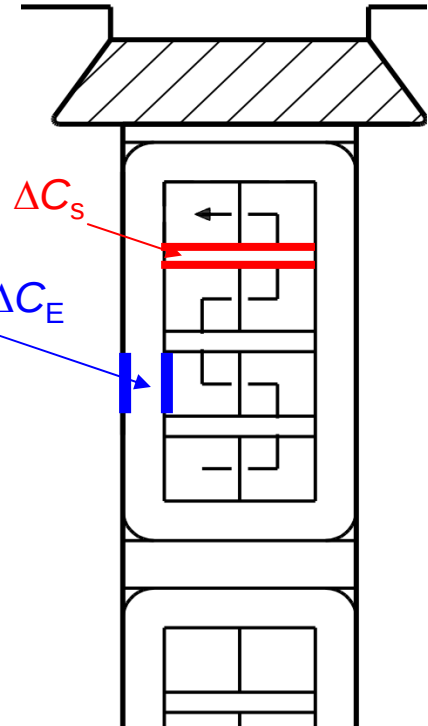

$$\gamma l = \sqrt{\frac{C_E'}{C_s'}} \cdot l = \sqrt{\frac{\Delta C_E}{\Delta C_s}} \cdot \frac{l}{\Delta x} = \sqrt{\frac{\Delta C_E}{\Delta C_s}} \cdot N_s$$

Although $\Delta C_E < \Delta C_s$, the parameter γl is big due to N_s !



Non-linear voltage distribution at “voltage step” ($du/dt \rightarrow \infty$)

Differential equation for line-to-earth voltage u_E :

$$\frac{d^2 u_E(x)}{dx^2} - \frac{C_E'}{C_s'} u_E(x) = 0$$



Boundary conditions: $u_E(x=0) = U_d$, $u_E(x=l) = 0$

Solution:

$$u_E(x) = U_d \cdot \frac{\sinh(\gamma \cdot (l-x))}{\sinh(\gamma \cdot l)}, \quad t=0$$

$$\gamma = \sqrt{C_E' / C_s'}$$

$$\text{unit } [\gamma] = 1/m$$

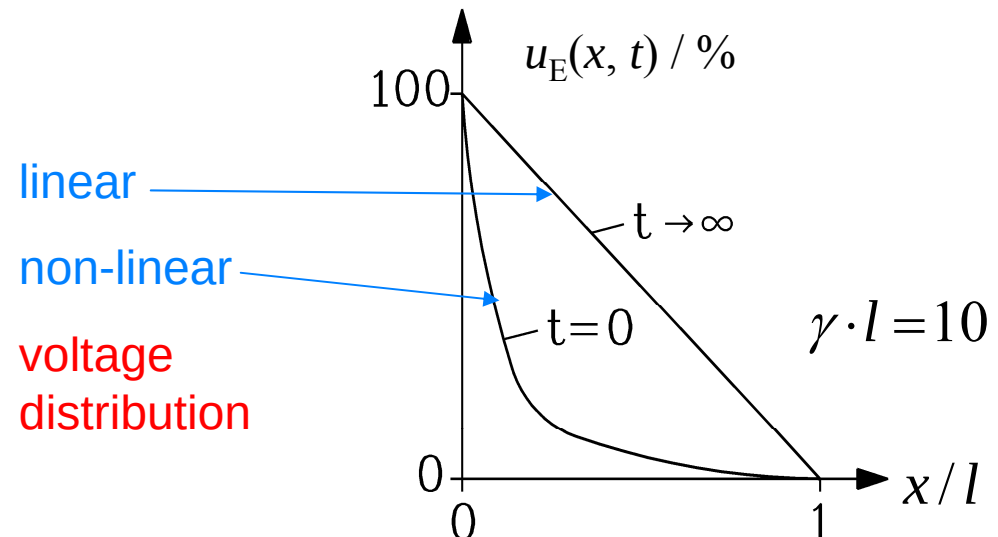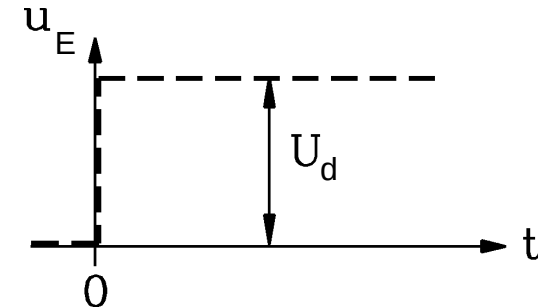


Oscillation of non-linear voltage distribution between $t = 0$ and $t \rightarrow \infty$

- Voltage distribution shortly after applying the voltage step **is only determined by winding capacities**

- Winding inductance, capacitance, resistance cause a **voltage oscillation**, which starts at non-linear distribution $u_E(x, t = 0)$ and ends at linear distribution $u_E(x, t \rightarrow \infty)$
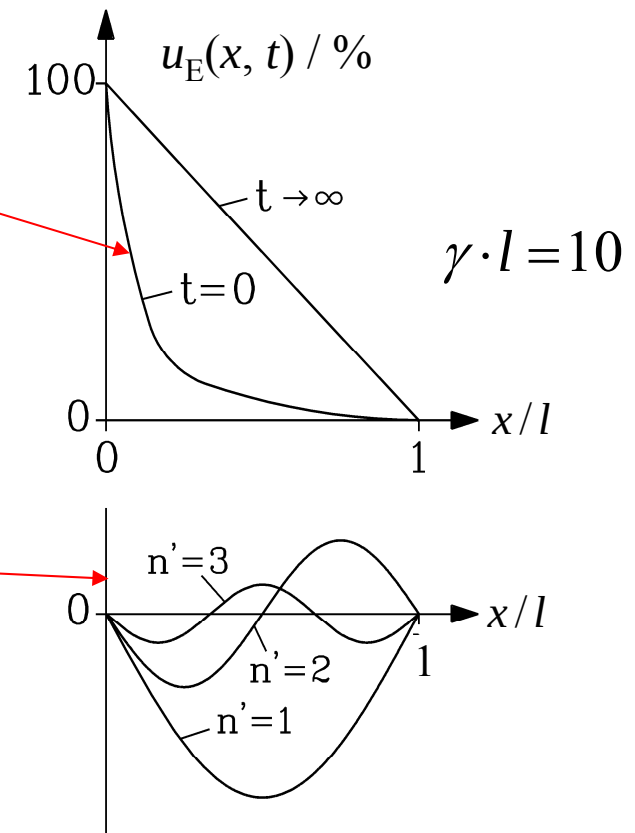
$$u_E(x, t) = \sum_{n'=1,2,\dots}^{\infty} \hat{U}_{n'} \cdot \cos\left(\frac{n' \cdot \pi \cdot x}{l}\right) \cdot \cos(n' \cdot 2\pi \cdot f \cdot t) \cdot e^{-t/T_{n'}} + u_E(x, t \rightarrow \infty)$$




Source: Heller-Veverka, VEB-Verlag Technik, Berlin, 1957




1st coil receives highest transient voltage

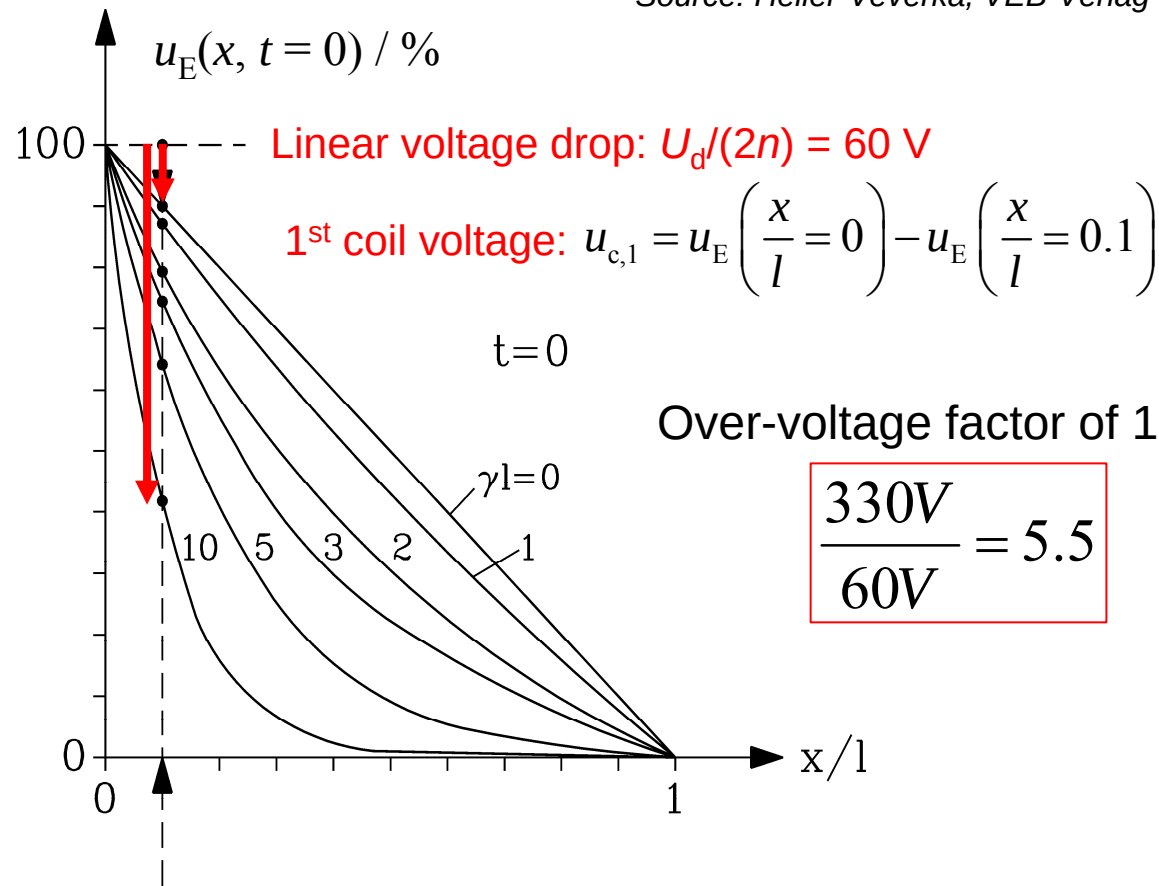Source: Heller-Weverka, VEB-Verlag Technik, Berlin, 1957



Over-voltage factor of 1st coil:


$$\frac{330\text{V}}{60\text{V}} = 5.5$$

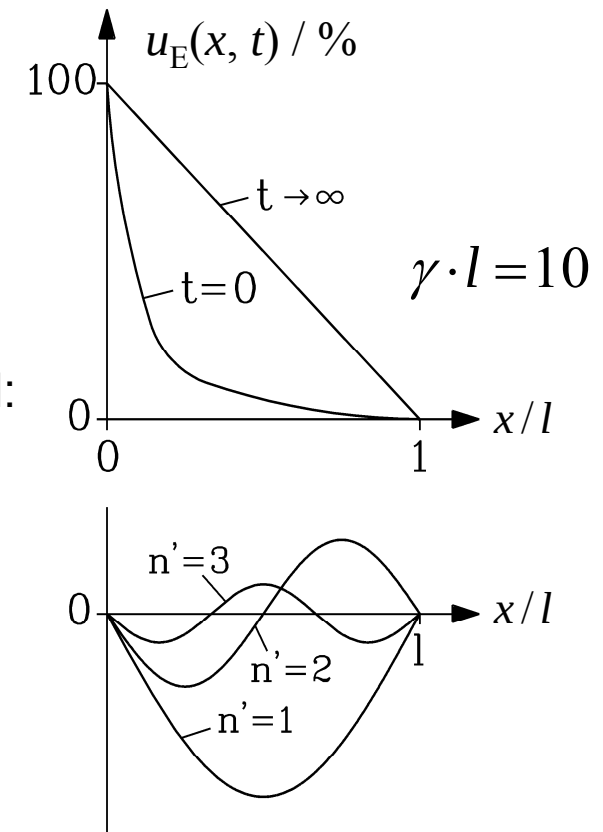

1st coil **Example:** Y-connected winding, $n = 5$ coils per phase, $2n = 10$ coils line-to-line,

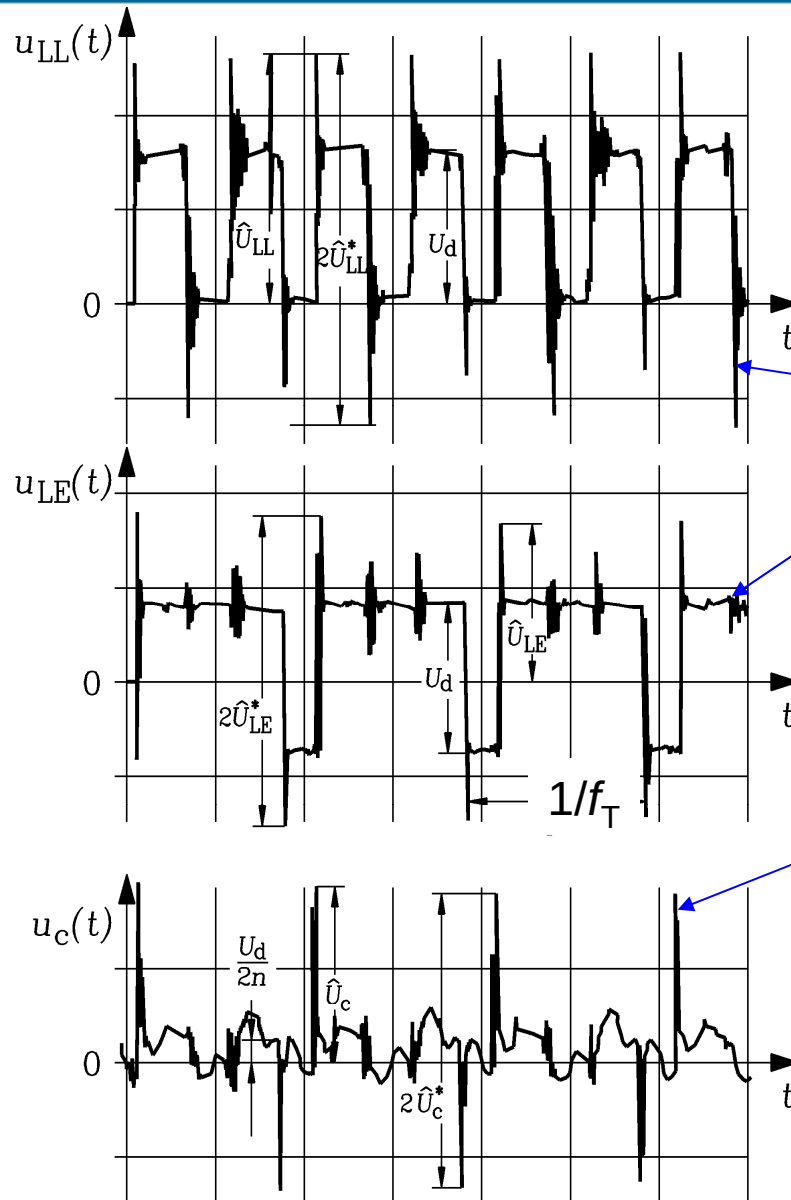$U_d = 600 \text{ V}$. 1st coil voltage: $u_{c,1}/U_d = 330/600 = 55\%$ of total voltage!





Measured motor terminal voltages at PWM IGBT-inverter operation

Hentschel E et al (1993): Beanspruchung der Wicklungsisolierung von Drehstrommaschinen. etz Vol. 114 No. 7: 1074-1077

Line-to-line terminal voltage

Line to earth terminal voltage

- 400 V Y-cage induction motor
- DC link voltage $U_d = 600$ V
- $l_c = 30$ m cable length between motor and inverter


Voltage drop at first coil per phase (n coils per phase)



Measured voltage at 1st coil per phase

Hentschel E et al (1993): Beanspruchung der Wicklungsisolierung von Drehstrommaschinen. etz Vol. 114 No. 7: 1074-1077

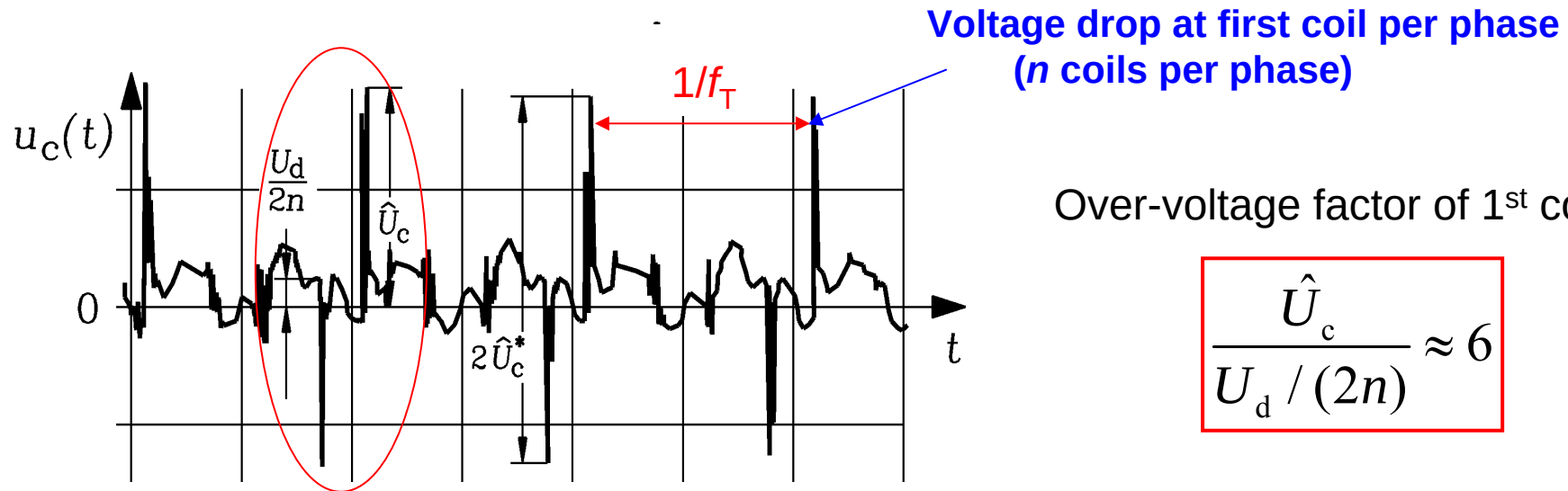- 400 V Y-cage induction motor
- DC link voltage $U_d = 600$ V
- $l_c = 30$ m cable length between motor and inverter



High frequency effects in inverter-fed AC electric machinery

Summary: HF voltage distribution in armature winding

- High du/dt causes big influence of capacities within winding on voltage
- Non-linear voltage distribution in the winding at high du/dt
- Increased insulation stress of the first winding turns at the incoming wave



High frequency effects in inverter-fed AC electric machinery

- 1 Voltage wave reflections at motor terminals
- 2 HF voltage distribution in armature winding
- 3 Insulation stress of AC winding at inverter supply
- 4 Parasitic HF currents
- 5 System design of inverter drives coping with big du/dt



Insulation stress due to high du/dt

- Steep voltage surges with high repetition rate cause locally high electric field strength usually in voids of the insulation system
 - ⇒ Local high electric fields cause ignition of small sparks (“partial discharges”)
 - ⇒ Ignition and extinguishing of local small sparks cause electric erosion of the insulation system with a final collapse of the insulation by direct flash-over
- High frequency electric fields within the healthy insulation cause also increased hysteretic polarisation losses (“dielectric losses”), but the loss density (W/m^3) is much too small to cause a dangerous temperature rise

Result:

Insulation stress at high du/dt due to partial discharges, not due to increased dielectric losses




Insulation stress due to partial discharges

- Local electrical field strength $E = dU/dx$ in voids of the winding insulation may cause a small sparks („partial discharge“)
- This **local arcing**, if occurring for long, destroys finally the insulation and causes a short-circuit e.g. between winding and housing

$E_{av} = U/d$: average electrical field strength

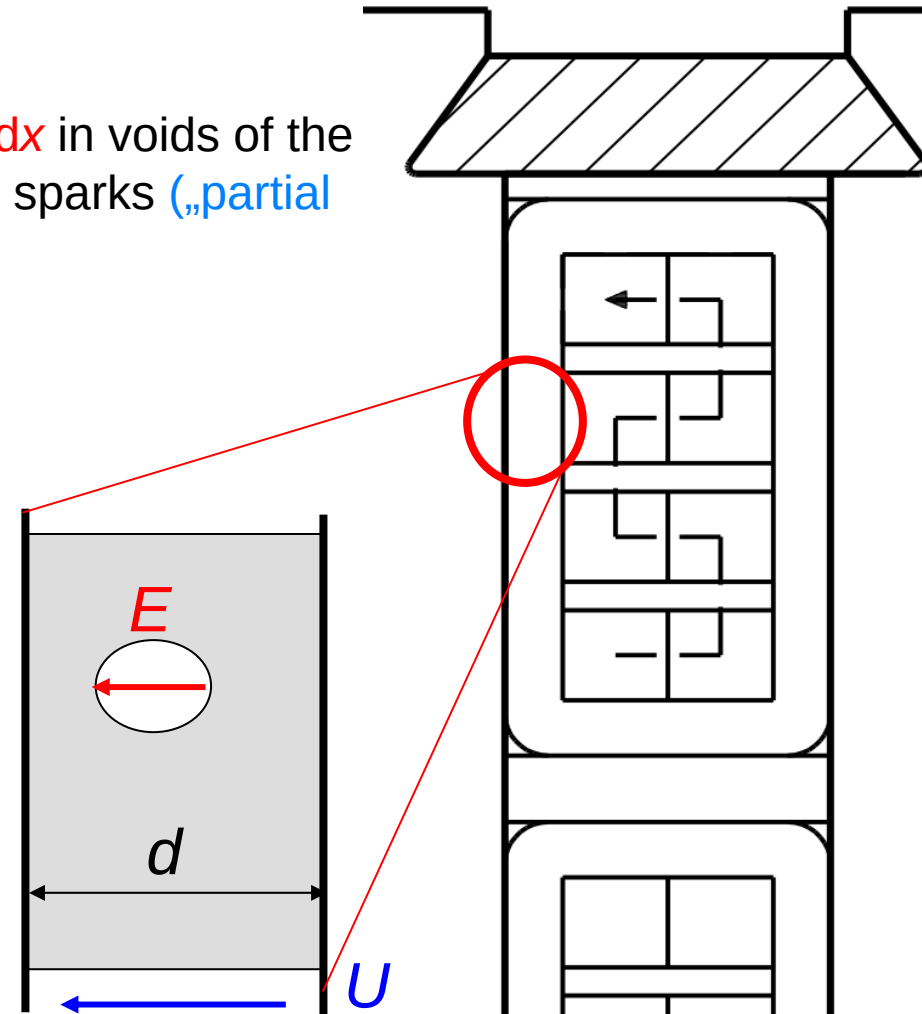$E > E_{av}$: local electrical field strength



Insulation stress of AC winding at inverter supply

Each voltage impulse may cause small spark ignition at weak points (e.g. voids)

- a) between the phases,
- b) between line and earth.

Small sparks = "**partial discharges (PD)**" are too faint to be visible, but repeated very often they will cause erosion of enamel, leading finally to a big flash over.

Note: Low voltage windings ($U_N < 1$ kV) with round wire (randomly distributed in the slots) and resin impregnation **may not resist for long** partial discharges.

Hence they must be kept **FREE** of partial discharges!



Partial discharge inception voltage U_{pd}

- At the **partial discharge inception voltage U_{pd}** the sparks start to ignite
- For low voltage resin-insulated round enamel coated wire windings:
PD inception voltage decreases with increasing winding temperature by ca. **4 V/K**
- **Thermal Class F motor:** Winding temperature ca. 150 °C :
 U_{pd} (50 Hz, r.m.s) at 20 °C: 1200 V $\rightarrow$ 1180 V at 150 °C

$$20^{\circ}\text{C} : U_{pd} = 1200\text{V}, \hat{U}_{pd} = U_{pd} \cdot \sqrt{2} = 1700\text{V} \Rightarrow$$

$$150^{\circ}\text{C} : \hat{U}_{pd} = 1700 - 4 \cdot (150 - 20) = 1180\text{V}$$


- Peak motor line-to-line voltage with full wave reflection $r_{mot} = 1$:

$$\frac{\hat{U}_{LL,mot}}{\hat{U}_N} \cong \frac{(1+r_{mot}) \cdot U_d}{U_d} = 2.0 \quad \hat{U}_{LL,mot} = 2 \cdot U_d = 2 \cdot 560\text{V} = 1120\text{V} < \hat{U}_{pd} = 1180\text{V}$$

Result: The motor winding is **safe** against du/dt -voltage stress !



Partial discharge test of stator winding

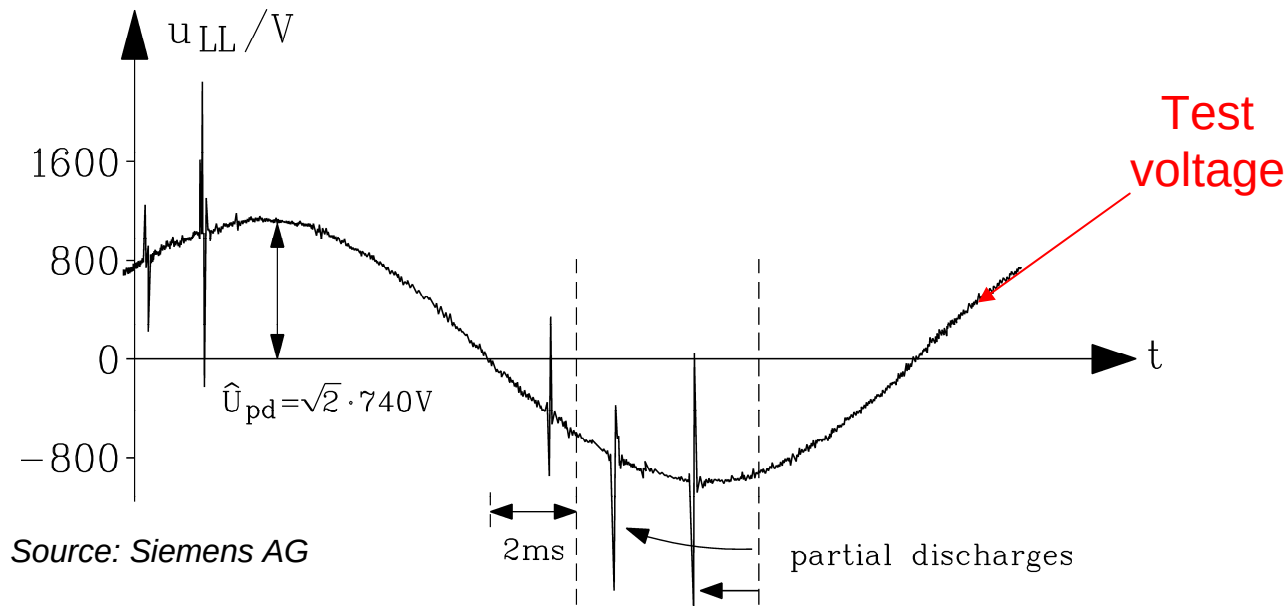


Test object: 2-pole 400V Y, 50 Hz, synchronous reluctance motor at 20 °C:

Test voltage: Sine wave, 50 Hz, line-to-line, variable amplitude, between the isolated phases U, V, W

- Spark discharge currents flow as HF spikes from one phase to the other.
- Via a HF capacitor this current flow is detected, being visible as additional HF voltage, superimposed on the test voltage



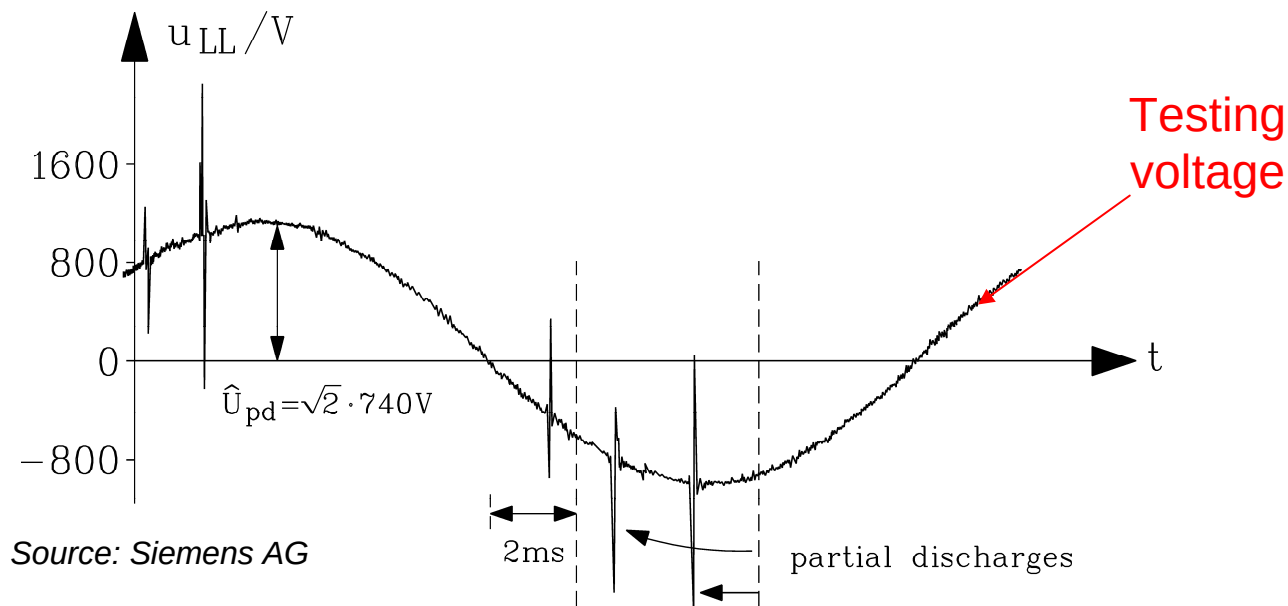Partial discharge test result of 3-phase stator winding




- Displaced inter-phase lining between phases U and V cause wire contact
- At line-to-line test voltage 740 V (r.m.s) partial discharges ignite at 20 °C
- Partial inception (PD) voltage $U_{pd} = 740 V$

Result: U_{pd} too low for safe operation at $U_d = 600 V$ with reflections!



Line-to-line terminal voltage

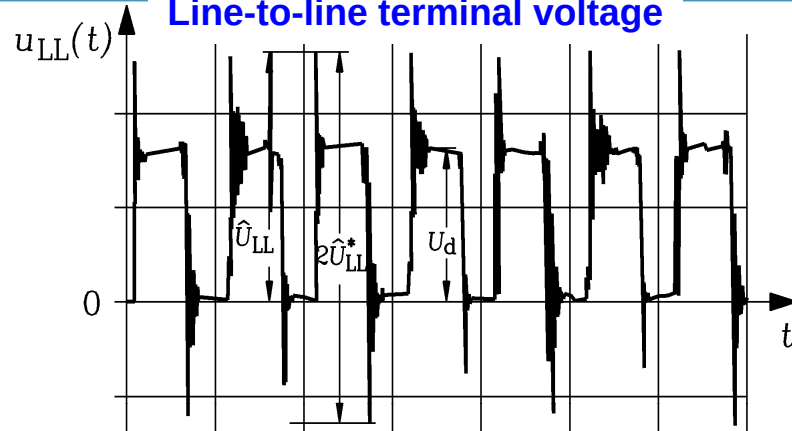

PWM motor terminal voltage parameters


DC link voltage: U_d

Motor line-to-line voltage amplitude:

$$\hat{U}_{LL} = (1 + r_{\text{mot}}) \cdot U_d$$


Pulse frequent AC line-to-line voltage amplitude: $2 \cdot f_T$
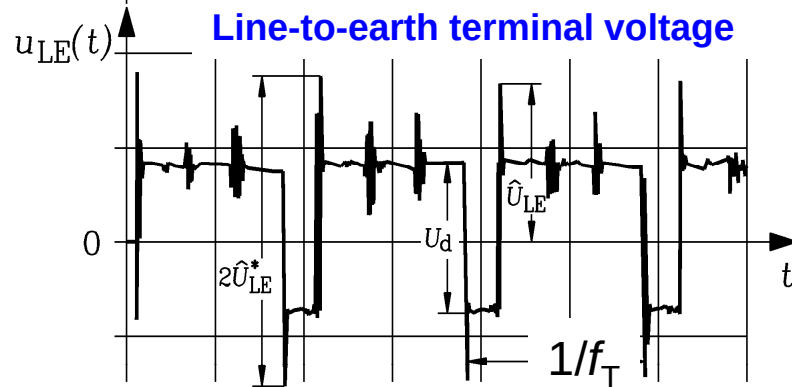
$$\hat{U}_{LL}^* = (0.5 + r_{\text{mot}}) \cdot U_d$$



Hentschel E et al (1993): Beanspruchung der Wicklungsisolierung von Drehstrommaschinen. etz Vol. 114 No. 7: 1074-1077

Voltage drop at 1st per phase

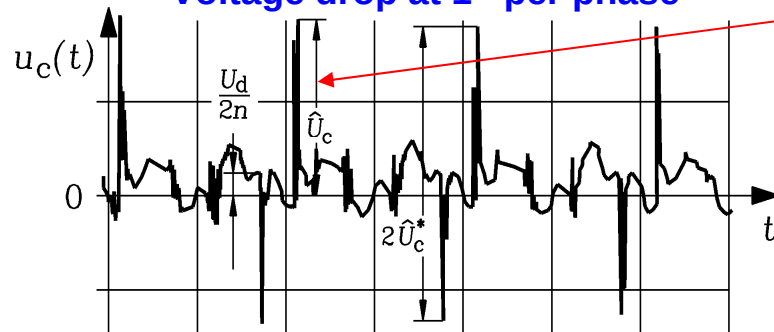

Amplitude of pulse frequent AC voltage of 1st coil per phase: $\hat{U}_c$



Motor winding voltage stress at PWM IGBT-inverter operation

Inverter input voltage	$U_{LL,grid}$	400 V	500 V
DC link voltage	$U_d \approx \sqrt{2} \cdot U_{LL,grid}$	565 V	710 V
Motor rated voltage	U_N	400 V	500 V
Motor line-to-line voltage amplitude	$\hat{U}_{LL} = (1 + r_{mot}) \cdot U_d$	1130 V	1420 V
Motor line-to-earth voltage amplitude	$\hat{U}_{LE} = (0.5 + r_{mot}) \cdot U_d$	850 V	1060 V
Pulse frequent AC line-to-line voltage amplitude ($2 \cdot f_T$)	$\hat{U}_{LL}^* = (0.5 + r_{mot}) \cdot U_d$	850 V	1060 V
Pulse frequent AC line-to-earth voltage amplitude ($2 \cdot f_T$)	$\hat{U}_{LE}^* = (0.5 + r_{mot}) \cdot U_d$	850 V	1060 V
Amplitude of pulse frequent AC voltage of 1 st coil per phase	e.g. a) $n = 6, k = 0.3$ b) $n = 6, k = 0.6$	290 V 630 V	365 V 790 V
<i>Hentschel E et al.: (1993) Elektrotechn. Zeitschrift etz Vol. 114 No. 7: 1074-1077</i>	$\hat{U}_c = \left[k \cdot (1 + r_{mot}) - \frac{1}{2n} \right] \cdot U_d$	$(r_{mot} = 1)$	$(r_{mot} = 1)$



High frequency effects in inverter-fed AC electric machinery

Summary: Insulation stress of AC winding at inverter supply

- Low voltage round wire windings suffer from partial discharges
- Partial discharges must be avoided in low voltage windings
- PD measurement necessary to assess admissible voltage limits



High frequency effects in inverter-fed AC electric machinery

- 1 Voltage wave reflections at motor terminals
- 2 HF voltage distribution in armature winding
- 3 Insulation stress of AC winding at inverter supply
- 4 Parasitic HF currents
- 5 System design of inverter drives coping with big du/dt



Parasitic HF currents



HF capacitive currents of cable and motor capacitances:

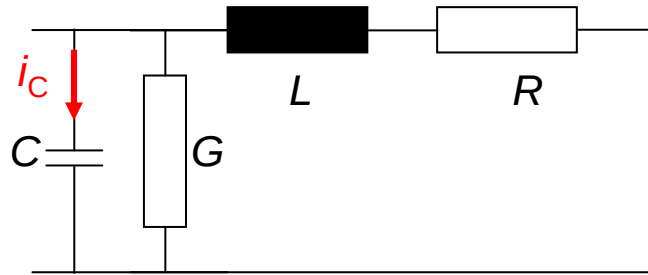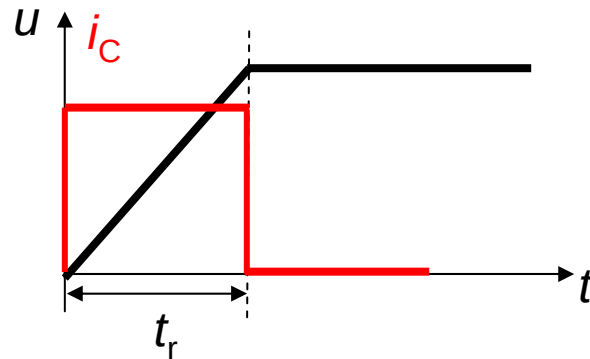- a) Capacitive **cable** current
- b) Capacitive **stator-to-ground current** via main insulation and earthed stator housing
- c) In case of rotor grounding: Capacitive **rotor-to-ground current** via bearings
- d) Capacitive currents within the motor e.g. via the bearings



Capacitive motor cable currents i_C

Simplified equivalent circuit of a cable with concentrated elements



$$i_C = C_{\text{cable}} \cdot \frac{du}{dt} \approx C_{\text{cable}} \cdot \frac{U_d}{t_r}$$

$$C_{\text{cable}} = C_c' \cdot l_c$$

Cable parameters:

L : inductance

R : ohmic resistance

C : capacitance

G : lossy insulation conductance

- Cable capacitance C_{cable}
 - increases with cable length l_c
 - depends on cable type (shielded / unshielded etc.)
- Long cables above 30 ... 50 m: HF reactive cable current i_C is big.
- **Inverter output chokes** limit i_C




HF capacitive parasitic currents within the motor

- Motor stray capacitances:
 - bearing lubricant film,
 - winding insulation
 - air gap between stator and rotor


Capacity of winding-to-ground: $C_E \approx C_{wh}$,

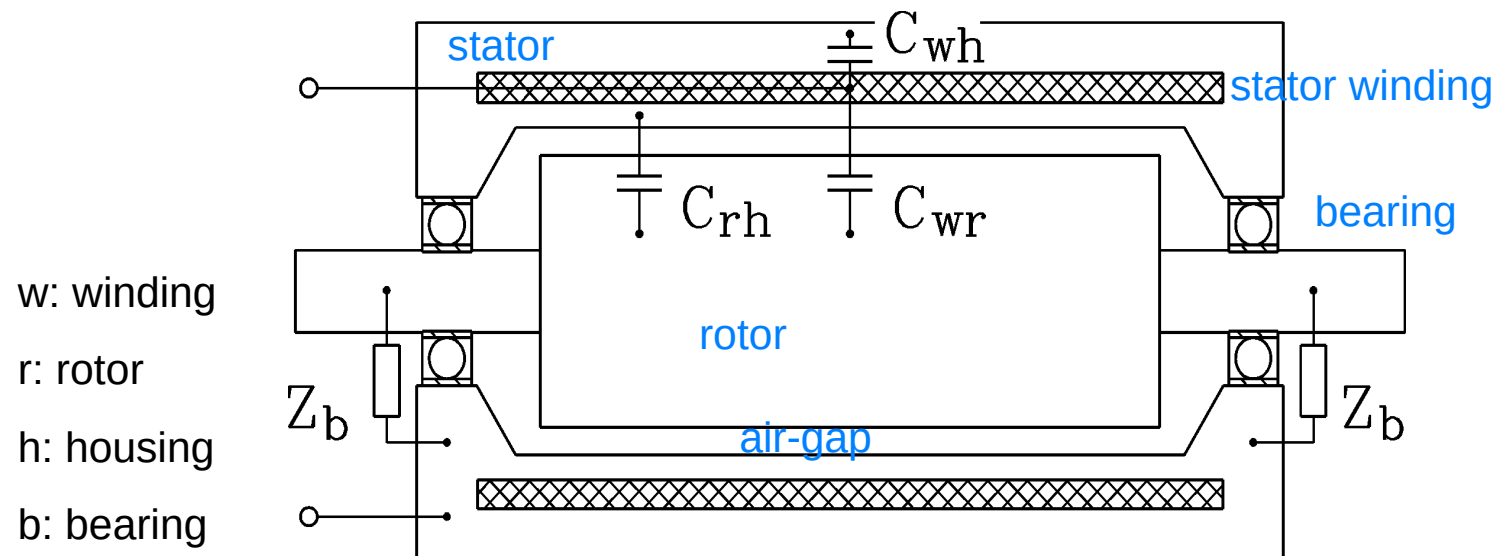Winding-to-rotor C_{wr} , rotor-to-housing C_{rh} , bearing C_b are ca. 100 times smaller!




Definition of common mode voltage u_0
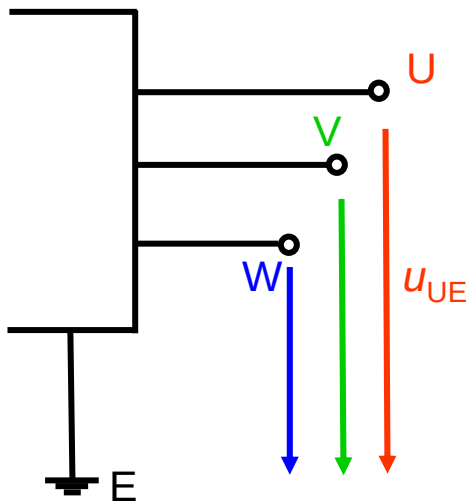
$$u_0(t) = \frac{u_{UE}(t) + u_{VE}(t) + u_{WE}(t)}{3}$$



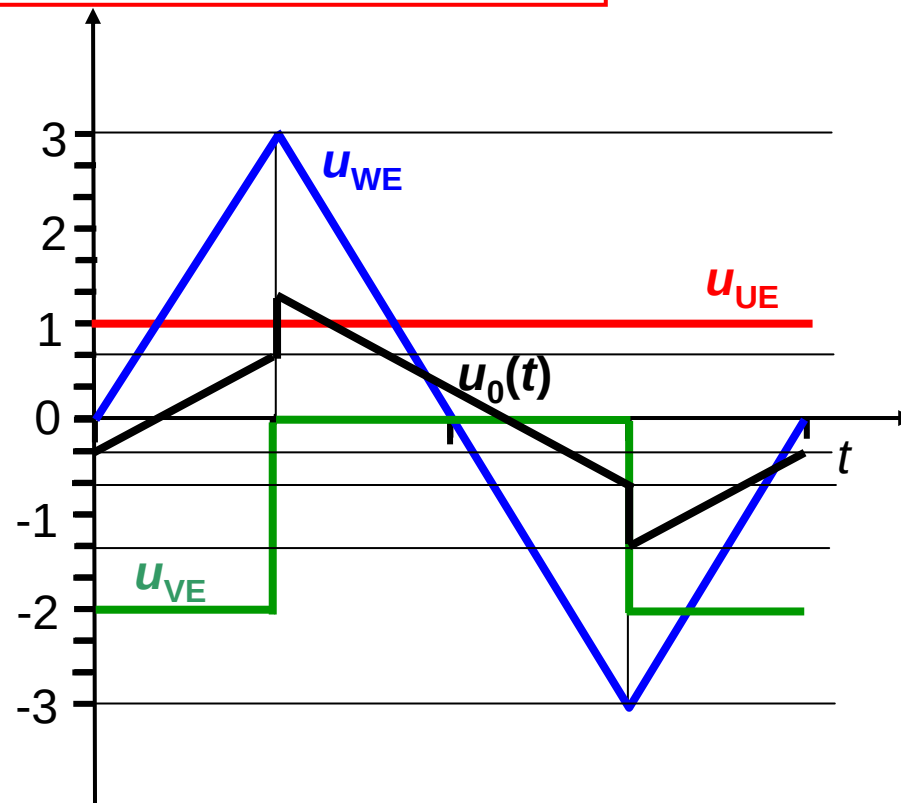Arbitrary line-to-ground voltages u_{UE} , u_{VE} , u_{WE} lead to the time-dependent common mode voltage u_0



Common mode inverter output voltage u_0

$$u_0(t) = \frac{u_{UE}(t) + u_{VE}(t) + u_{WE}(t)}{3}$$


Two-level PWM inverter: Output potential is either $+U_d/2$ or $-U_d/2$

Common mode voltage u_0 :

- is either $U_d/6$, $-U_d/6$, $U_d/2$, $-U_d/2$

- values change with switching frequency f_T

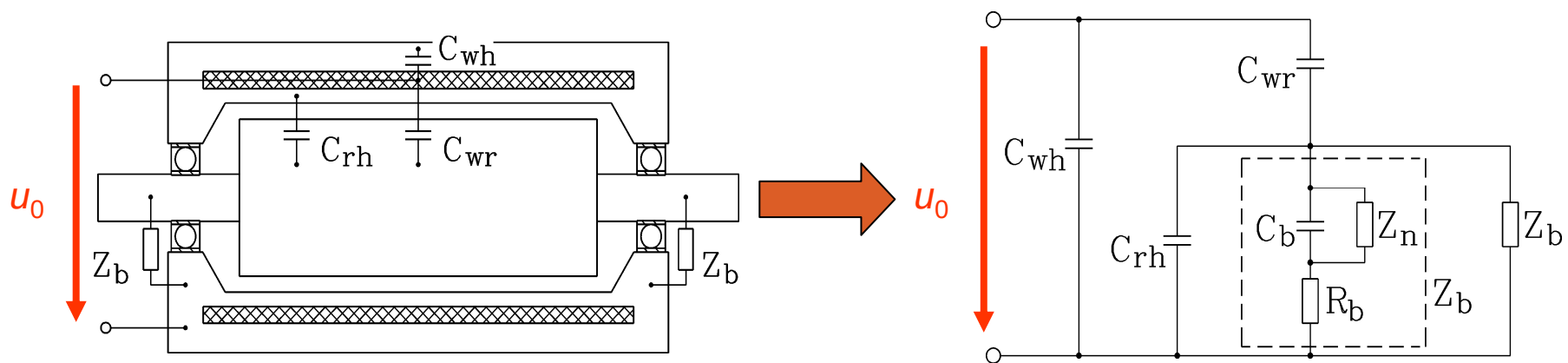
du/dt of common mode voltage causes HF parasitic motor currents:



Motor capacitive equivalent circuit



HF stator-to-ground current i_g

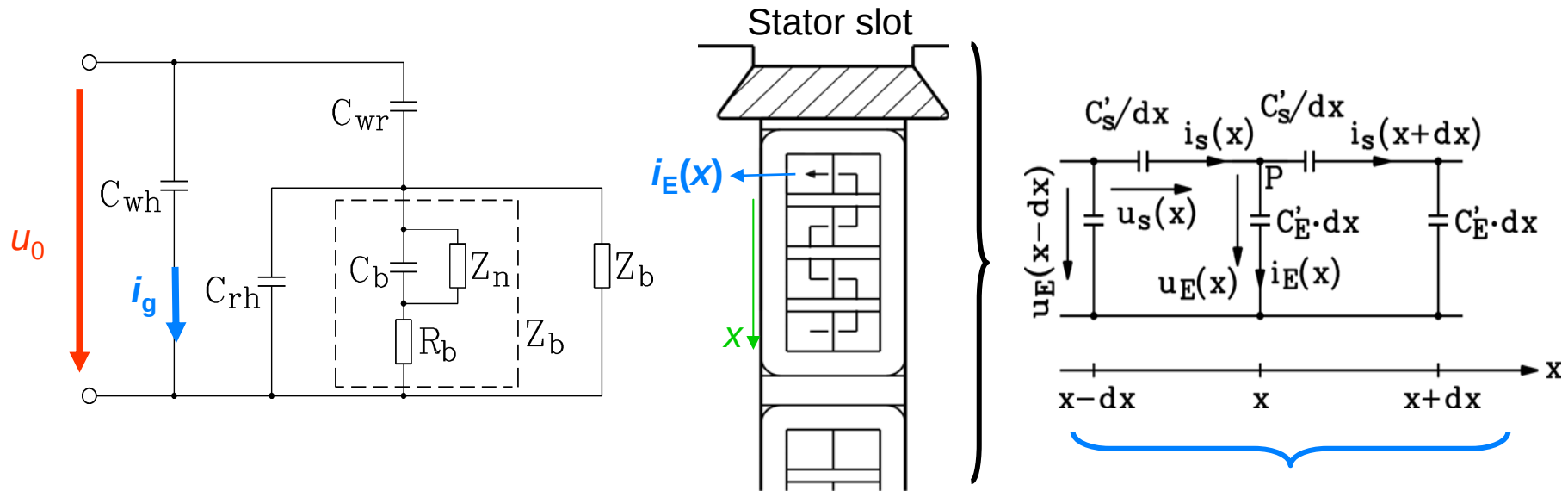

Stator-to-ground current:

$$\int i_E(x) \cdot dx / l = i_g$$

Via series and ground capacities C_s , C_E of series turns per coil the earth current distribution $i_E(x)$ is integrated along the length l of the winding, yielding the **stator-to-ground current i_g**




Measured common mode stator-to-ground current i_g





Test bench for measurements of CM currents at a 240 kW induction motor

240 kW, 4 pole cage induction motor


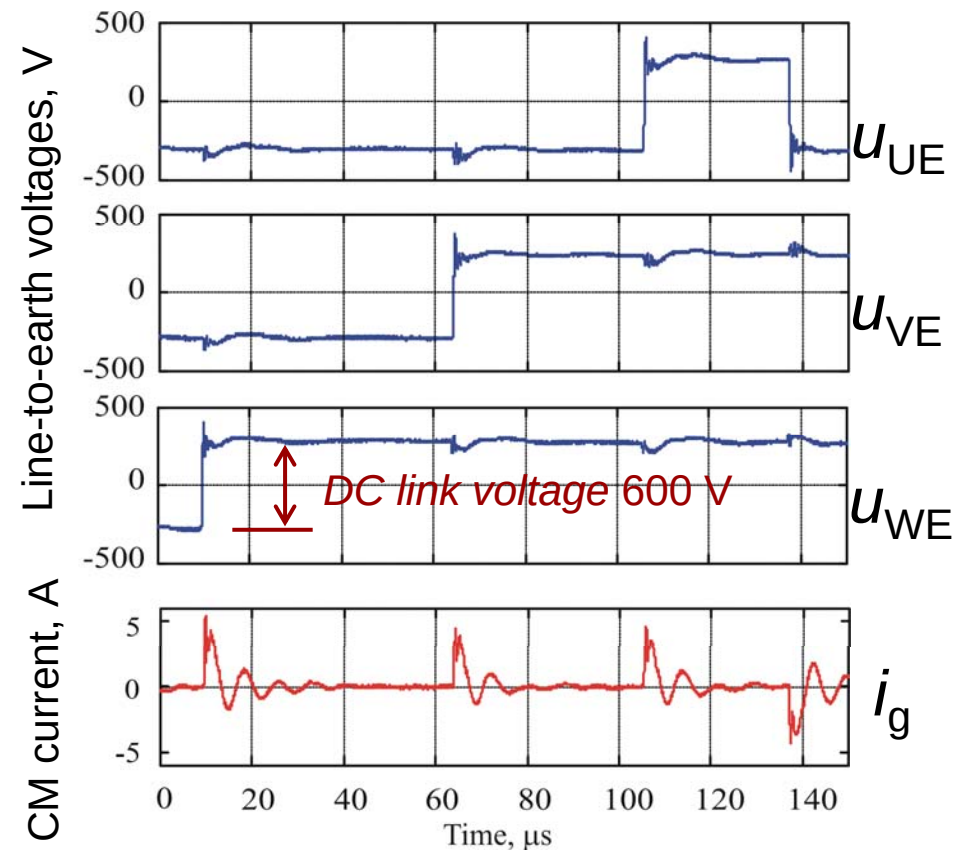


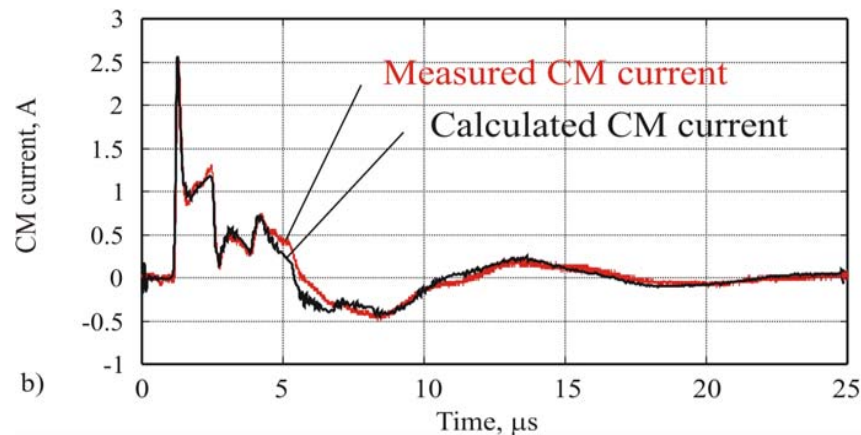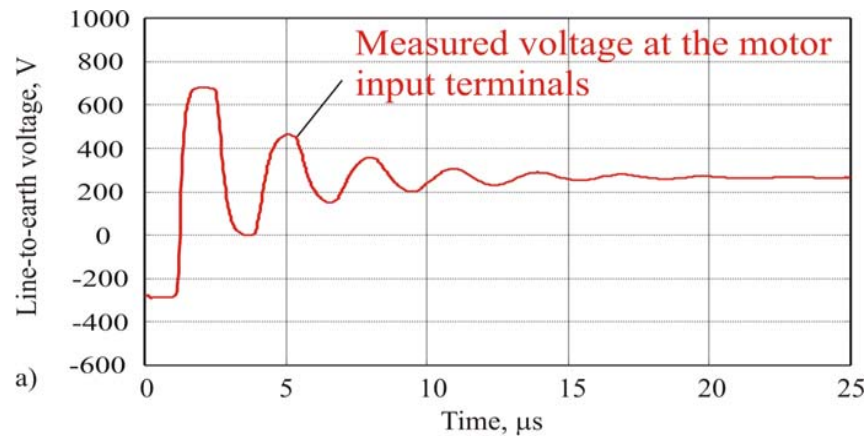Measured HF stator-to-ground currents i_g



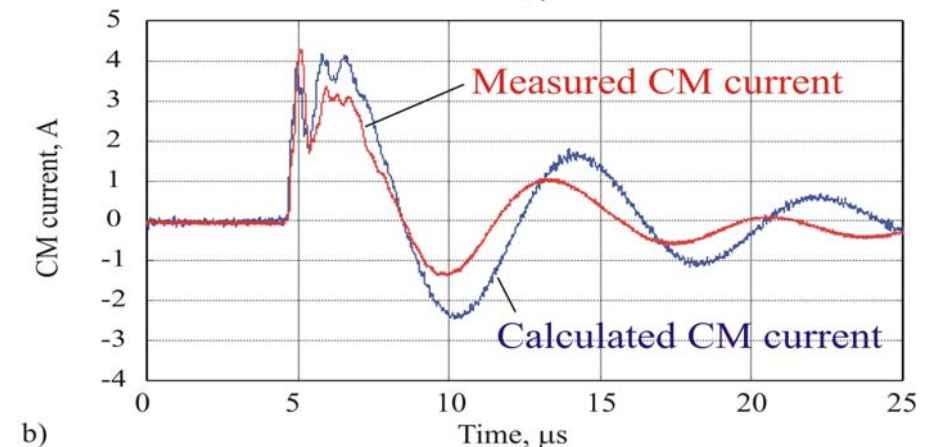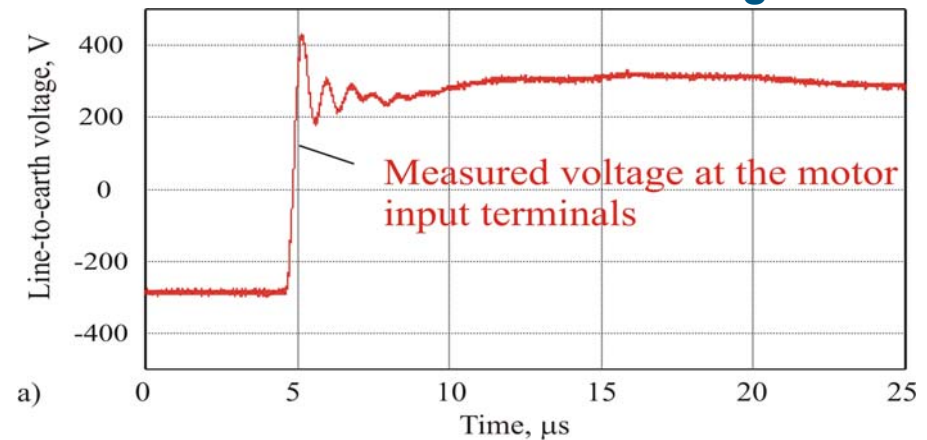7.5 kW induction motor,
 motor cable length $l_c = 100$ m,
 DC link voltage $U_d = 560$ V,
 $f_T = 3$ kHz switching frequency

Source: O. Magdun,
 PhD Thesis,
 TU Darmstadt



240 kW induction motor,
 motor cable length 2 m,
 DC link voltage 560 V,
 4 kHz switching frequency




Parasitic HF bearing common mode voltage u_b

Intact insulating bearing lubrication film: $Z_n \rightarrow \infty$
 Common mode voltage u_0 is causing
 a common mode bearing voltage u_b
 over the bearings by a capacitive voltage divider!
 (Bearing resistance R_b small!)

$$BVR = \frac{u_b}{u_0} \cong \frac{C_{wr}}{C_{wr} + C_{rh} + 2 \cdot C_b}$$

BVR: bearing voltage ratio
 $BVR \approx 0.03 \dots 0.1$

Motor: Equivalent capacitive HF circuit

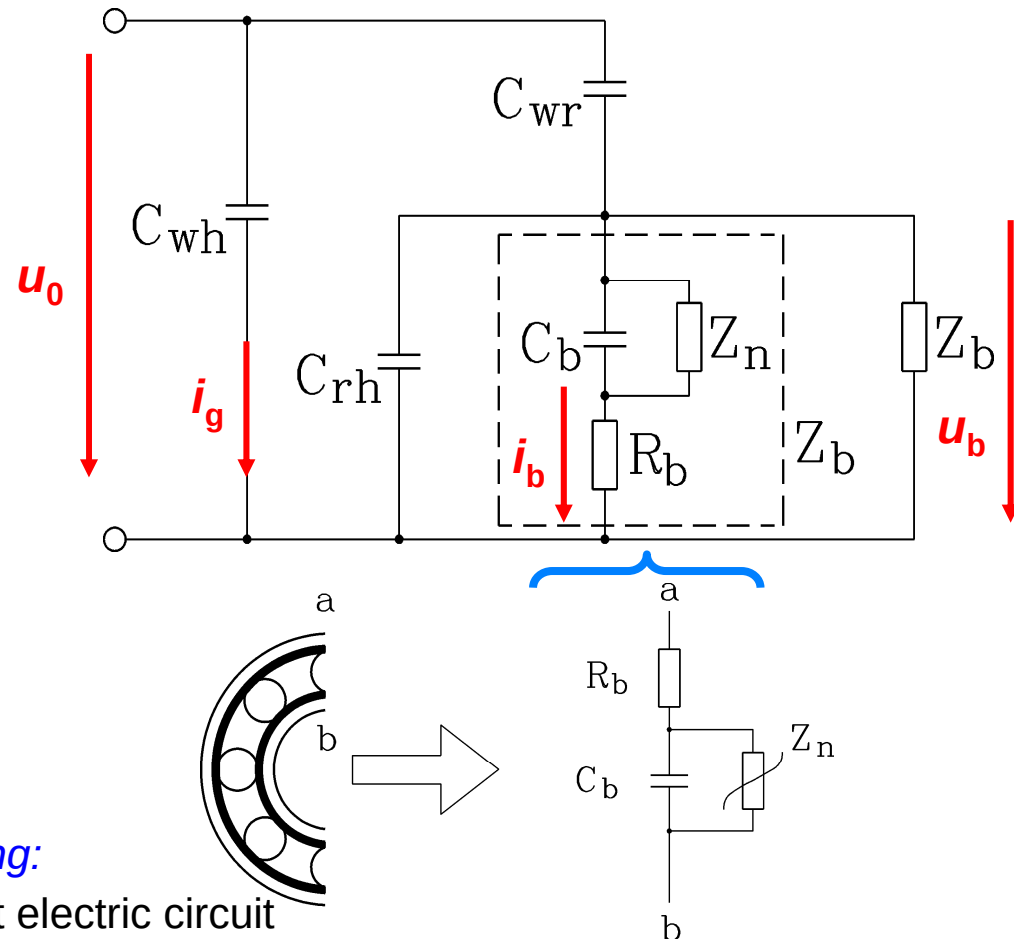

Ball bearing:

Equivalent electric circuit



Electric field strength E_b in intact lubrication film

$$BVR = \frac{u_b}{u_0} \cong \frac{C_{wr}}{C_{wr} + C_{rh} + 2 \cdot C_b} \approx 0.03 \dots 0.1$$

$$u_b = u_0 \cdot BVR = \left(\frac{U_d}{6} \dots \frac{U_d}{2} \right) \cdot (0.03 \dots 0.1)$$

$$U_d = 600V: \quad u_b \approx (100 \dots 300) \cdot (0.03 \dots 0.1) = 3 \dots 30V$$

Intact insulating bearing lubrication film thickness $h_0 \approx 0.5 \dots 3.0 \mu m$
(depending on speed, temperature, load, lubricant, ...)

$$E_b = u_b / h_0 \approx (3 \dots 30V) / (0.5 \dots 3 \mu m) = 1 \dots 60 kV/mm$$

At a typical threshold value of $E_D = 15 kV/mm$ a short electric arc discharges the lubricant, causing a discharge bearing current $i_{b,EDM}$ ($Z_n \rightarrow 0$)

This discharge bearing current $i_{b,EDM}$ deteriorates the bearing race surface by electric erosion ("Machining") (EDM: electric discharge machining)



Capacitive parasitic HF bearing currents i_{bC}


Intact insulating bearing lubrication film: $Z_n \rightarrow \infty$:
bearing behaves as capacitance C_b

$$i_{bC} = C_b \cdot \frac{du_b}{dt} = C_b \cdot BVR \cdot \frac{du_0}{dt}$$

Small values $C_b \approx 50 \dots 200 \text{ pF}$, depending on bearing size, type, load, temperature,

$$C_b = 200 \text{ pF}, U_0 = U_d / 2 = 300 \text{ V}, t_r = 100 \text{ ns} : i_{bC} = 200 \text{ pF} \cdot 0.1 \cdot (300 \text{ V} / 100 \text{ ns}) = 60 \text{ mA}$$

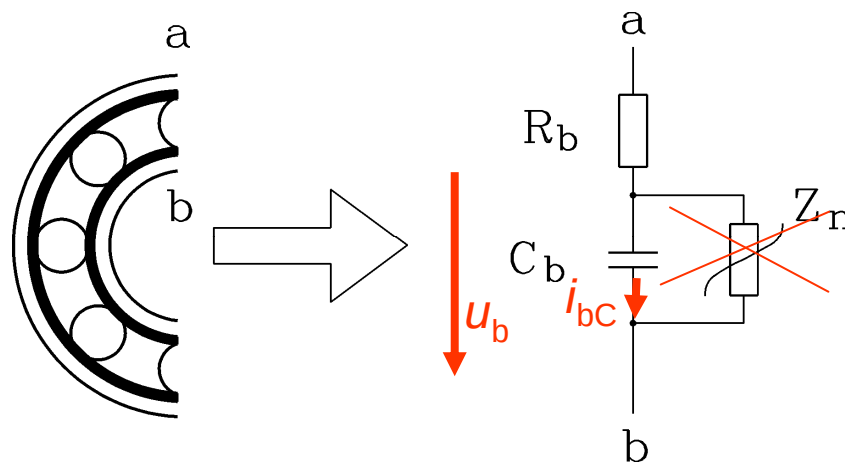Small & harmless capacitive bearing currents in the mA-range




Ball bearing:
Equivalent electric circuit




Electric discharge bearing currents $i_{b,EDM}$

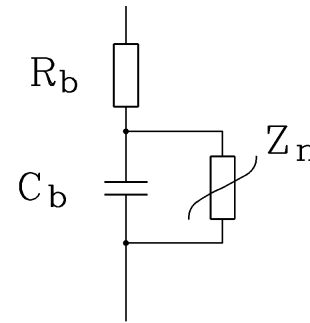Bearing lubrication film acts as a “switch”:




Intact film: $Z_n \rightarrow \infty$

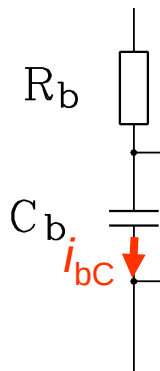

$E_b < 15 \text{ kV/mm}$

Capacitive parasitic HF bearing currents i_{bC}

Punched film: $Z_n \rightarrow 0$

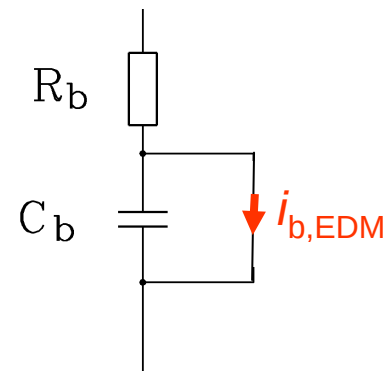


$E_b > 15 \text{ kV/mm}$

Electric discharge parasitic HF bearing currents $i_{b,EDM}$



Measurement of EDM current: Induction motor 240 kW

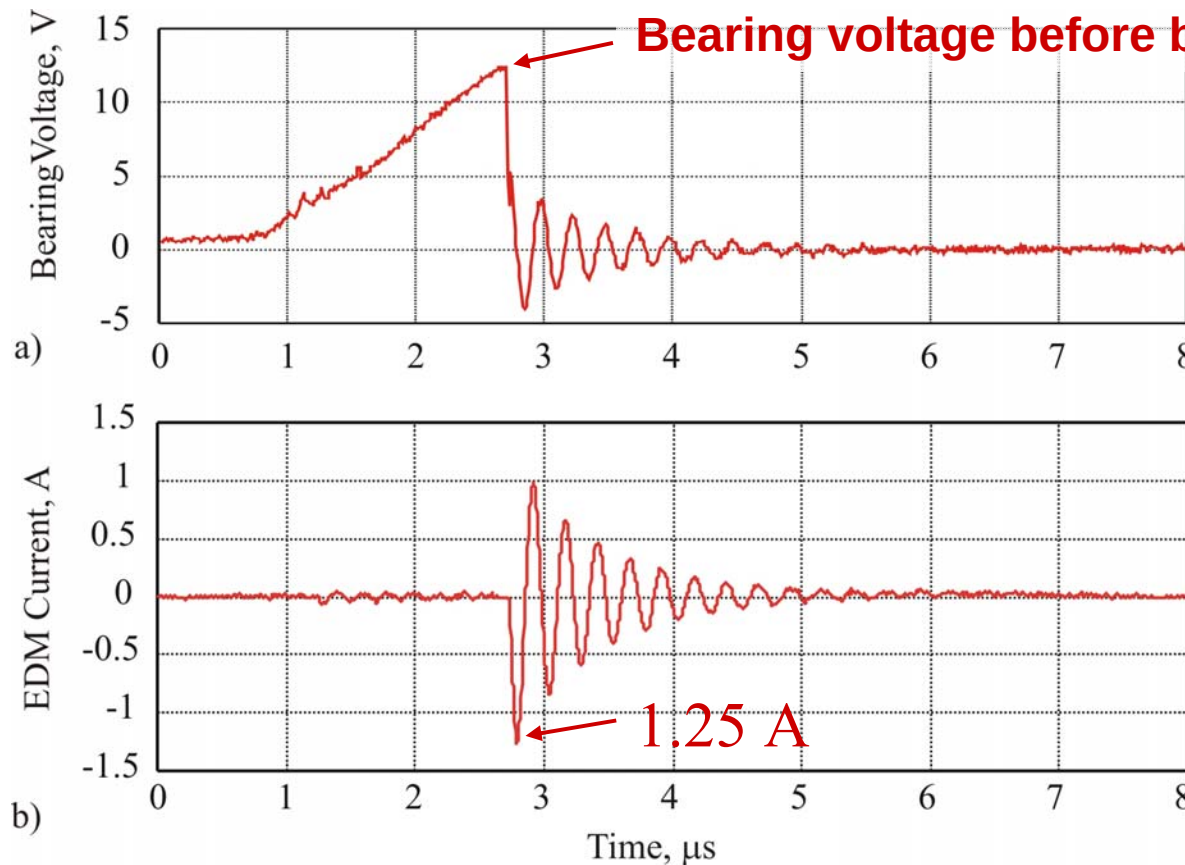Bearing voltage (a) and EDM current (b) at a speed of **300 rpm** of the **240 kW induction motor**, $f_T = 4 \text{ kHz}$ switching frequency, DC link 600 V



$$\hat{u}_b = 12.5 \text{ V}$$

Lubricant thickness:
estimated for a typical
threshold value of **15 kV/mm**

$$h_c \cong 0.8 \mu\text{m}$$

$$\hat{i}_{b,\text{EDM}} = 1.25 \text{ A}$$



Effects of discharge bearing currents $i_{b,EDM}$

Discharge of lubricant film: Craters at race and ball surface



Crater due to short arcs

Source: SKF bearing catalogue, 1997

$$\hat{i}_b / A_{\text{Hertz}} < 0.3 \text{ A/mm}^2$$

Small currents $i_{b,EDM}$ $\Rightarrow$ Small craters are usually levelled by the rolling elements, yielding a **grey and stable race track**

The lubricant is not destroyed


$$\hat{i}_b / A_{\text{Hertz}} > 0.6 \text{ A/mm}^2$$

Big currents $i_{b,EDM}$ $\Rightarrow$ Bigger craters ($\varnothing$ 1... 5 μm) may cause the rolling elements to “jump” over the crater rim, causing a “hitting pattern” (fluting) behind the craters.

Fluting of the race track in the loading zone of the bearing causes increased friction heat = over-heating of the lubricant, which is destroyed, leading to a bearing failure.



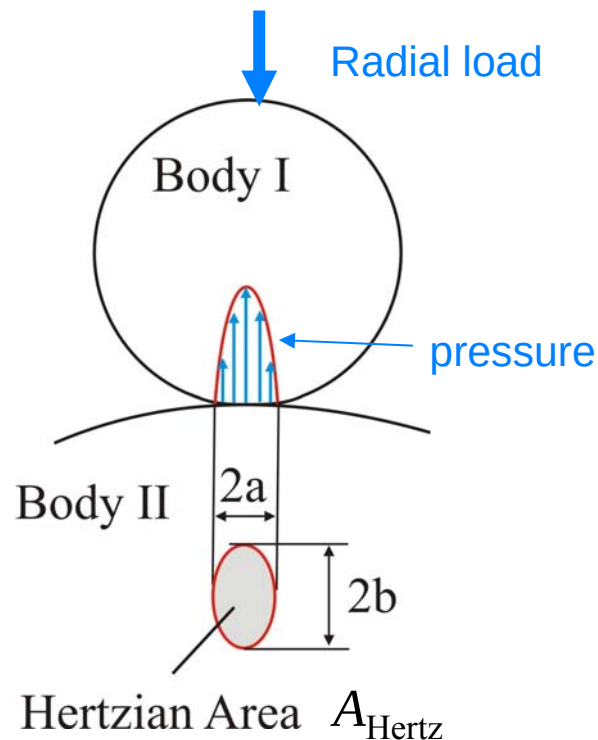HERTZian area of elastic deformed roller element under radial load



Apparent bearing current J_b :

$$J_b = \frac{\hat{i}_b}{A_{\text{Hertz}}}$$



Micro-craters on the ball surface due to small arcs



Due to the micro-craters the ball surface does not mirror any more!



Ball with craters

Ball without craters

Source: Brenner, Bürstadt,
Germany




TECHNISCHE UNIVERSITÄT DARMSTADT
Institute for Electrical Energy Conversion



Prof. A. Binder
57


ICEM
International Conference on Electrical Machines

Fluting due to bearing current

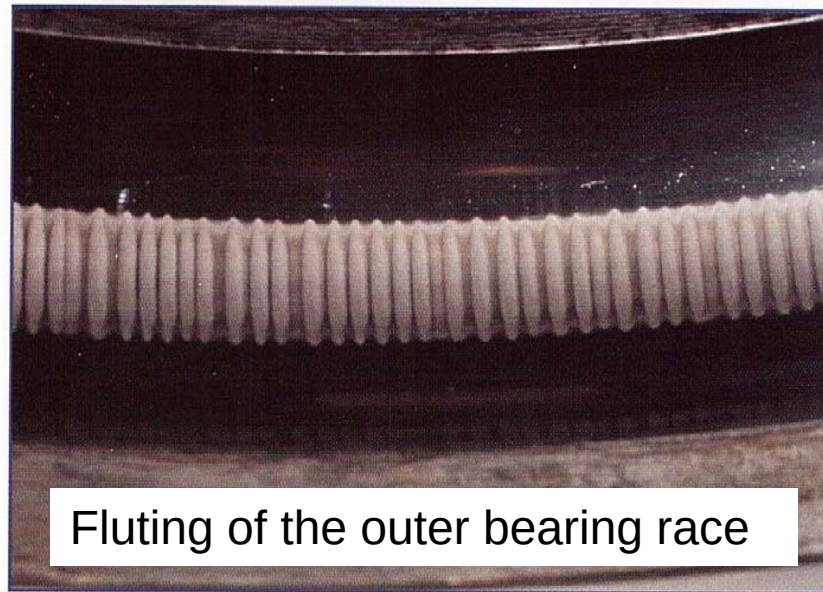

Source: Brenner, Bürstadt,
Germany


Fluting
in the bearing
load zone

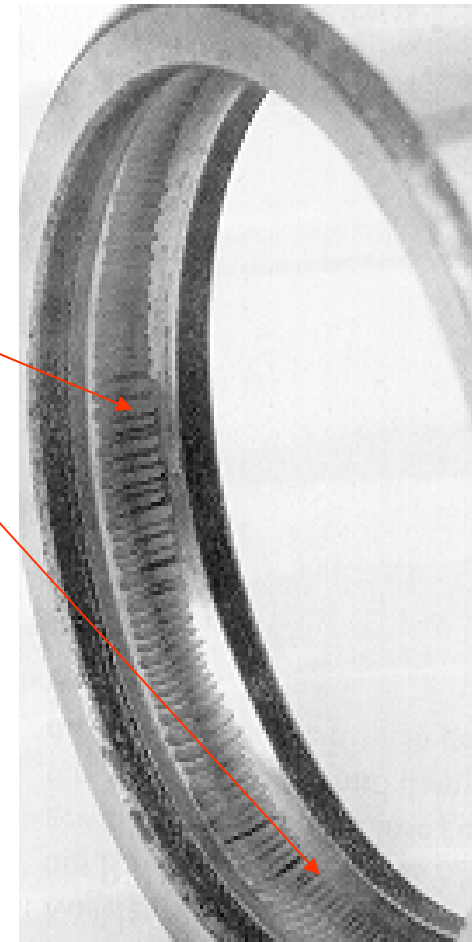

Source: SKF bearing catalogue, 1997



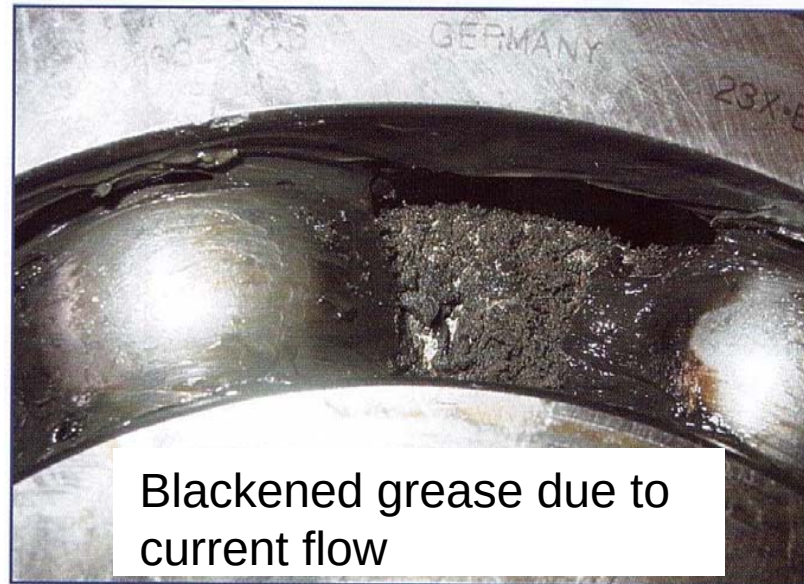Darkened grease lubricant due to bearing current





*Source: Brenner, Bürstadt,
Germany*



HF common mode ring flux Φ_c

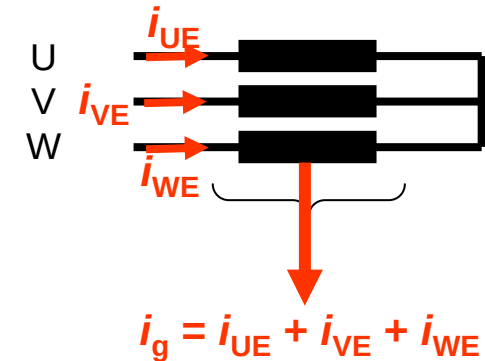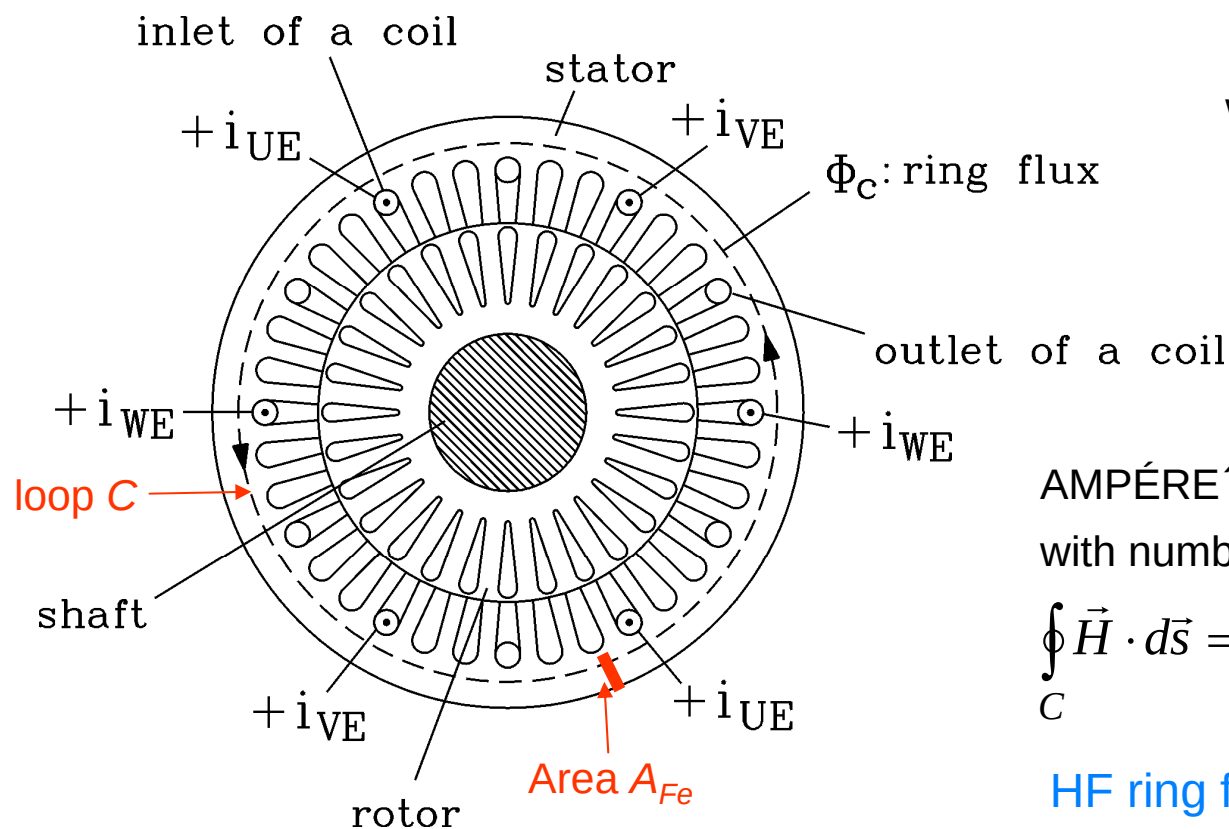The rather big **stator-to-ground current** i_g as per phase i_{UE} , i_{VE} , i_{WE} excites a HF “ring flux” Φ_c around the shaft



AMPÉRE's law along loop C:
with number of turns N_s


$$\oint_C \vec{H} \cdot d\vec{s} = N_s \cdot (i_{UE} + i_{VE} + i_{WE})$$

HF ring flux: $\Phi_c(t) = \mu_{Fe} \cdot H(t) \cdot A_{Fe}$

e.g.: 4 poles, 3 phases, $q = 3$ slots per pole & phase



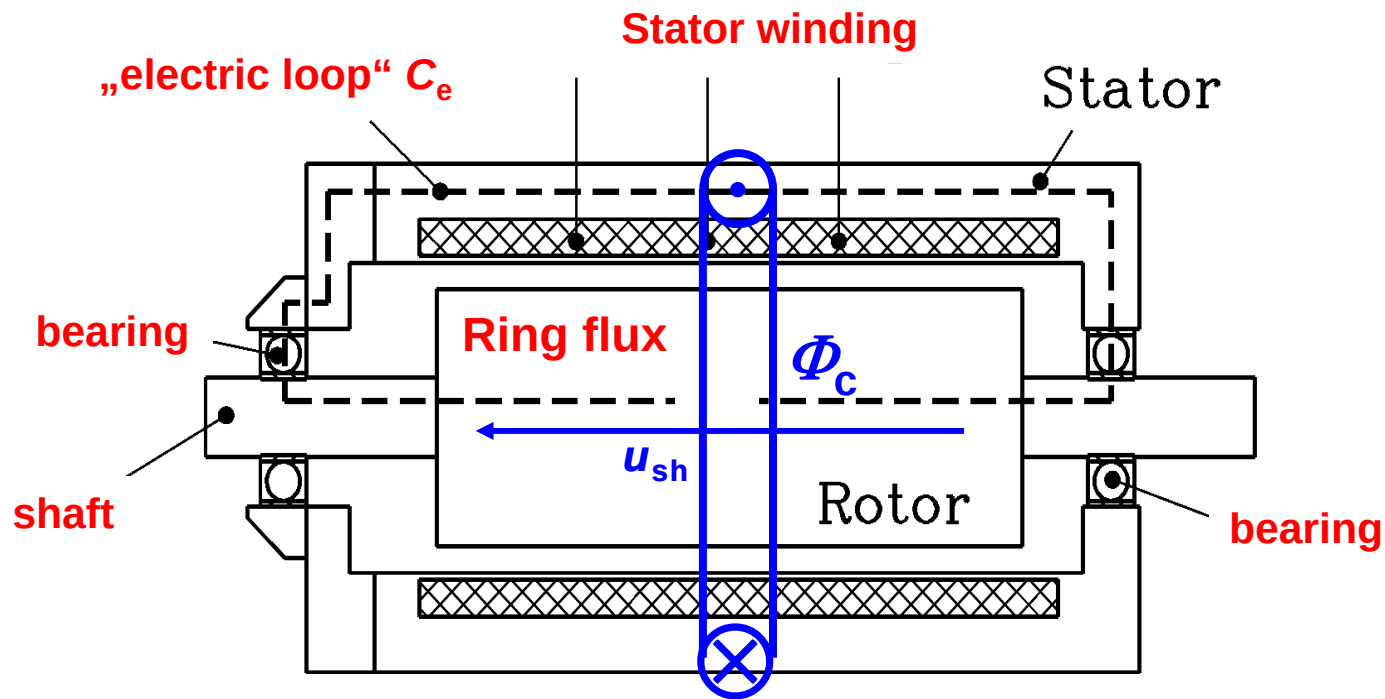HF common mode ring flux Φ_c induces shaft voltage u_{sh}



FARADAY's law along loop C_e :
$$u_{sh} = \oint_{C_e} \vec{E}_{sh} \cdot d\vec{s} = -d\Phi_c / dt$$

HF "ring flux" $\Phi_c(t)$ induces **shaft voltage** $u_{sh}(t)$ in the "loop" C_e of stator housing, bearings and rotor shaft

A circulating HF parasitic current $i_{b,circ}$ is driven by u_{sh} via the bearings!




Measured circulating HF bearing current $i_{b,circ}$

560 kW, 2 poles induction motor (s: stator, r: rotor, e: outer, i: inner)

$d_{se} = 680$ mm, $d_{si} = 360$ mm, $d_{re} = 353$ mm, $d_{ri} = 150$ mm, $l_{Fe} = 490$ mm

20 A/div

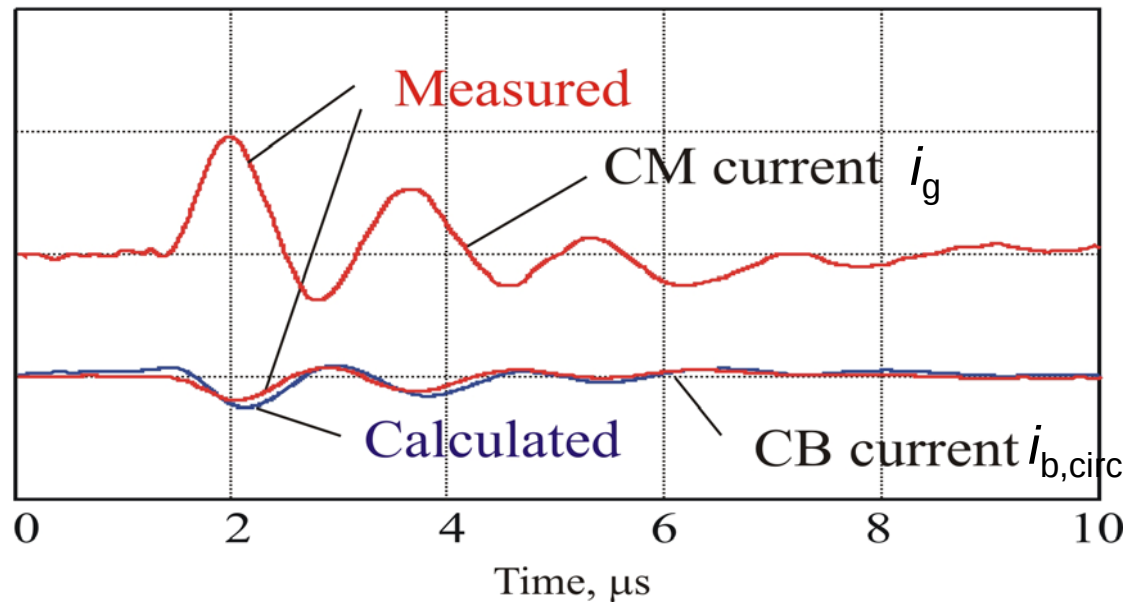

The *equivalent transformer circuit* is a harmonic circuit. Thus, the **FOURIER series** of the CM current waveform i_g is required to calculate $i_{b,circ}$

Sources:

A. Mütze & O. Magdun,
PhD Theses, TU Darmstadt

The stator-to-ground current i_g and the circulating bearing current $i_{b,circ}$ have due to *Ampère's* and *Faraday's* law the **same wave form!**



High frequency effects in inverter-fed AC electric machinery

Summary: Parasitic HF currents

- Capacitive common mode cable current due to PWM inverter
- Common mode voltage and current may cause bearing current flow
- Capacitive, discharge and circulating bearing currents



High frequency effects in inverter-fed AC electric machinery

- 1 Voltage wave reflections at motor terminals
- 2 HF voltage distribution in armature winding
- 3 Insulation stress of AC winding at inverter supply
- 4 Parasitic HF currents
- 5 System design of inverter drives coping with big du/dt




Short motor cable length to avoid voltage reflection

Combined inverter-induction motors

- Inverter on top of the motor (at the terminal box)
- Possible for small inverter power ratings (typically below 20 kVA)
- Short cable length between inverter and motor
- No extra inverter installation necessary (plug-and-play)

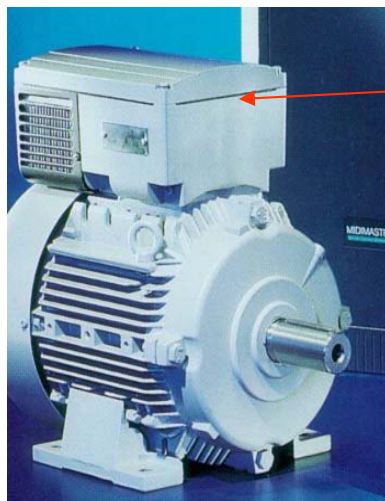BUT: Increased vibration and heat loading for the inverter




inverter

Source: Siemens AG

7.5 kW, 4-pole cage induction motor

Gear box

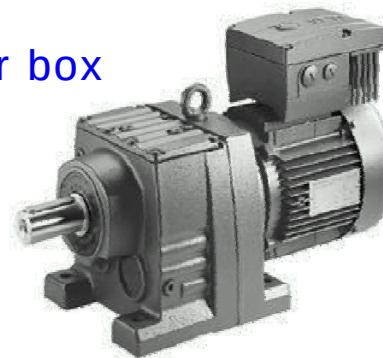


Motor+
Inverter

Source: SEW Eurodrive, Bruchsal, Germany

Combination of motor, inverter and gear box


Inverter self-cooling
via cooling fins

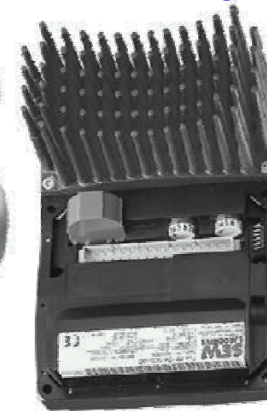

PM synchronous servo motors with integrated inverter

Combined inverter-PM synchronous motors

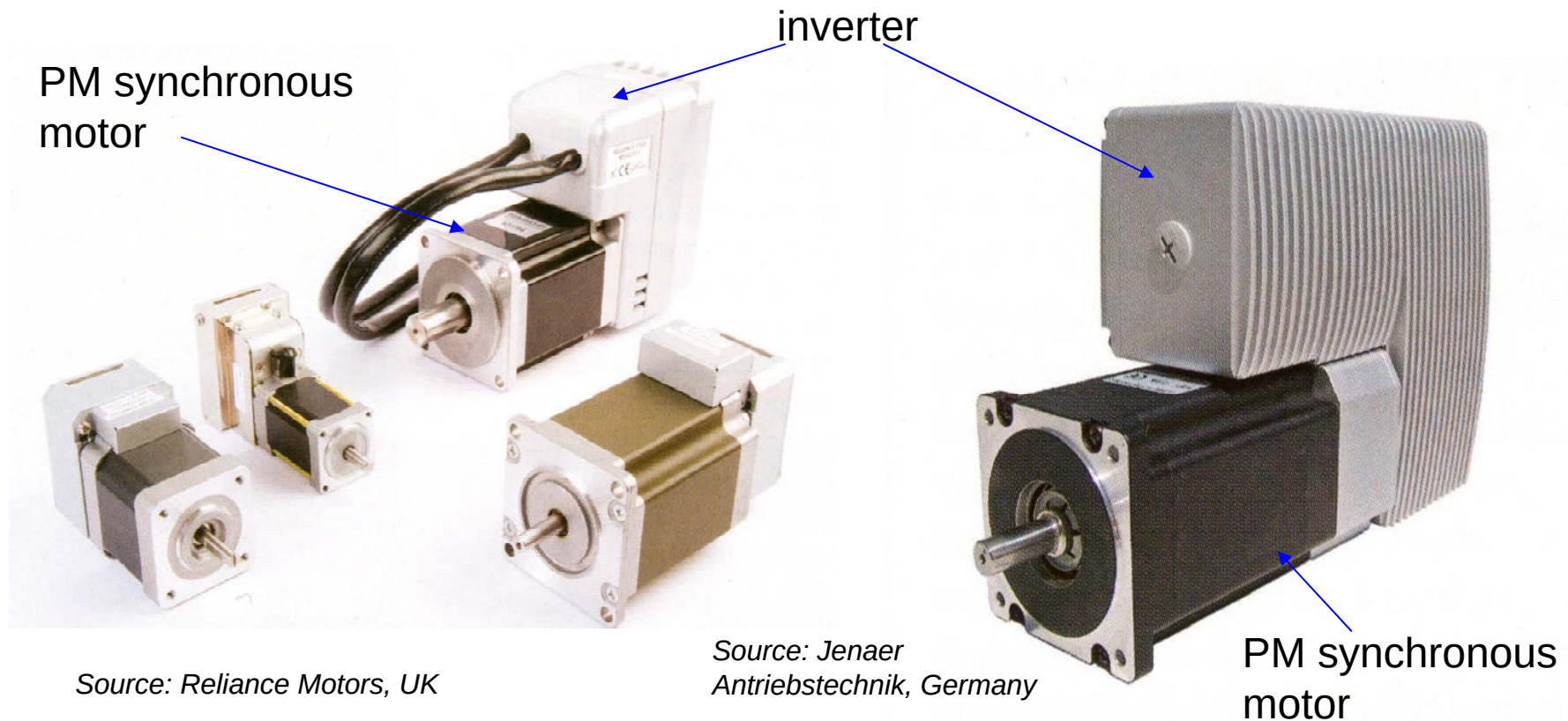- Inverter with DC link as input, so DC bus with only two terminals




Size limit of combined inverter-motors


Motor size determined by torque

Inverter size determined by power

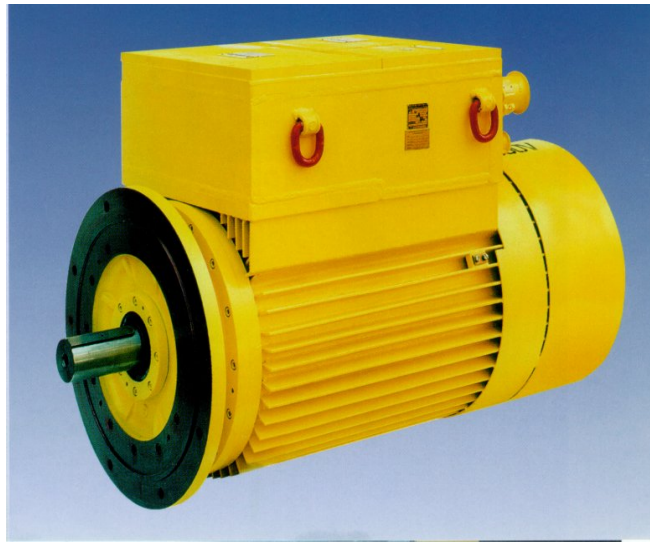- Low speed motors are big at small power, allowing a good integration of the small inverter into the big motor
- High speed: Small motors at big power rating do not allow a good inverter-motor combination



22 kW integrated inverter motor

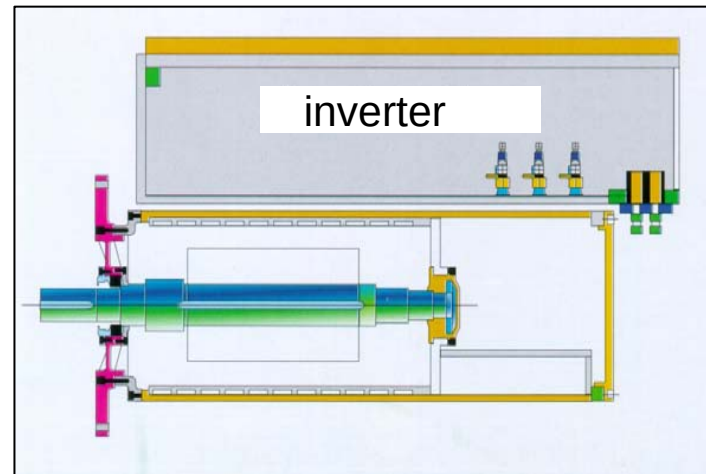


Source: Breuer, Germany



Reducing du/dt -effects for motor insulation stress via inverter output filter


du/dt -filter

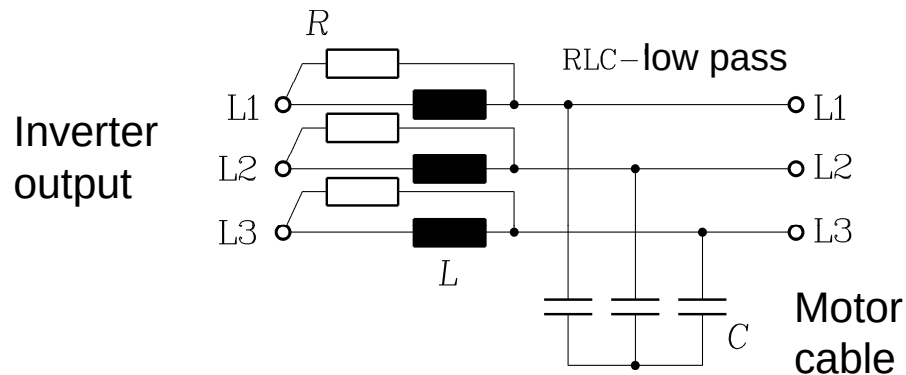L - C -combination with resonance frequency
ABOVE double switching frequency $f_{\text{res}} > 2f_T$
 $\Rightarrow$ Steep du/dt -slopes reduced
 $\Rightarrow$ Current switching ripple still active
(magnetic noise, add. losses, ...)



sine-wave filter

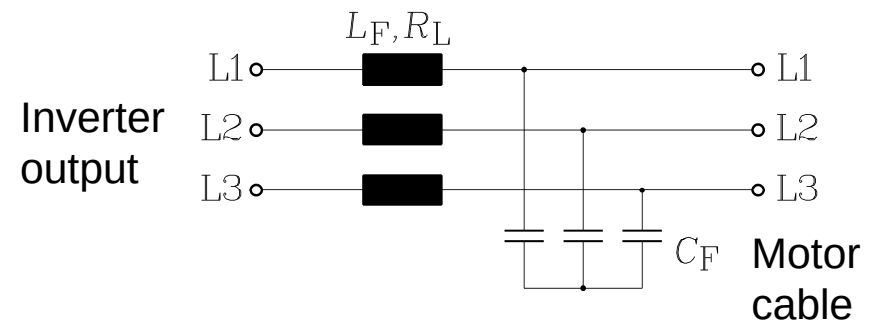L - C -combination with resonance frequency
above fundamental frequency $f_{\text{res}} > f_s$
 $\Rightarrow$ Nearly sinusoidal line-to-line voltage
 $\Rightarrow$ Current switching ripple removed
BUT: Much bigger size than du/dt -filter, more expensive




These filters do not suppress the common mode voltage u_0 !



Reducing the inverter common mode voltage u_0 via inverter output filter

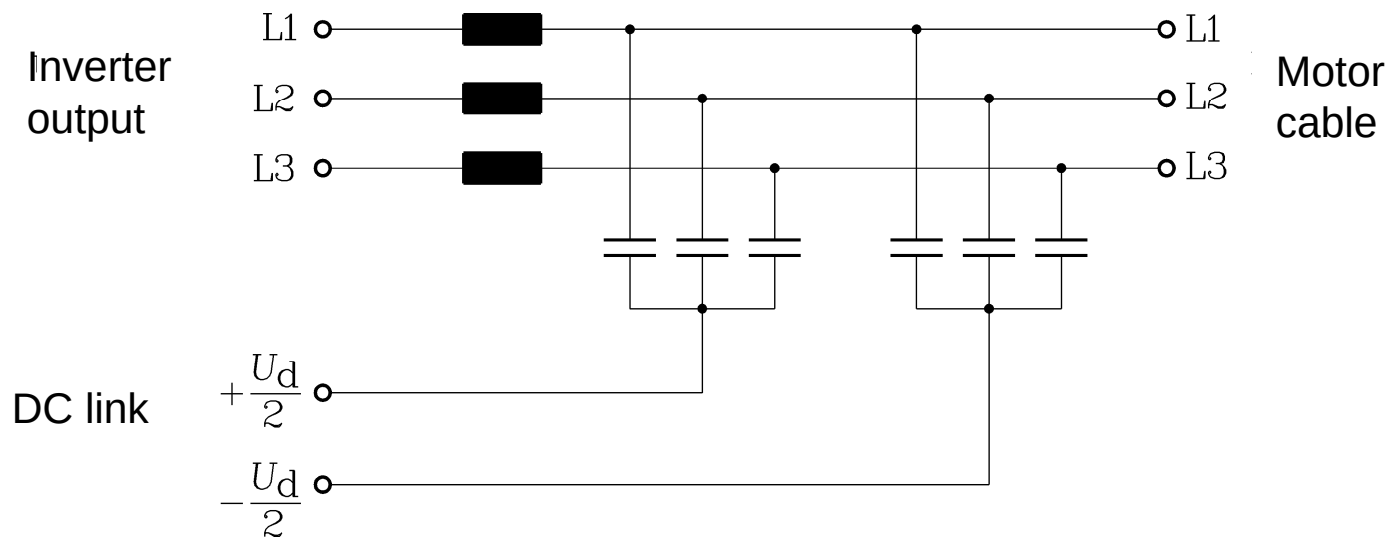- L-C-combination low pass filter with direct connection to the DC link to suppress the common mode harmonics
- Usually only for small power ratings available



This filter reduces all parasitic HF current effects in the motor, as the common mode voltage u_0 is reduced!



Measures to cope with HF parasitic motor currents

<i>Bearing current type</i>	<i>EDM current</i>	<i>Circulating current</i>	<i>Rotor-to-ground current</i>
dominantes at	Small motors: Frame size $\leq (132...160)$ mm	Bigger motors: Frame size $\geq (200...280)$ mm	Caused by low-impedance rotor grounding
<i>Motor cable: shielded or unshielded?</i>	No influence	Shielded: Increases circulating currents slightly	Shielded (= stator ground path): strong rotor ground current reduction
<i>CM voltage rejection filter</i>	Complete annihilation	Complete annihilation	
<i>du/dt-Filter, sine wave filter, CM HF current chokes</i>	No influence	Current reduction by (30 ... 90) %	
<i>Electrostatic shielding of stator winding</i>	Strong reduction	No influence	
<i>Low-impedance grease</i>	Strong reduction	Increase of bearing current	
<i>One insulated bearing</i>	Reduction there by (40...60) %	Reduction by 60 % ... 80 %	
<i>Hybrid bearings</i>	Complete annihilation	Complete annihilation	
<i>Shaft grounding brush</i>	Strong reduction	By-pass for bearing current; check overload of brush	



High frequency effects in inverter-fed AC electric machinery

Summary:

System design of inverter drives coping with big du/dt

- Many system parameters influence the HF performance
 - Grounding system (low impedance?)
 - Stator vs. rotor grounding (e.g. roller mill)
 - Cable shielding (grounding, EMI, ...)
- Filter technologies for Differential Mode and Common Mode voltages and currents available (limit for power ratings, additional costs)
- Motor design for low du/dt -voltage stress = high partial discharge inception voltage
- Motor design for low bearing currents (small motors: no circulating currents!)
- Low impedance grease and one insulated bearing as a good combination for reducing EDM and circulating currents



High frequency effects in inverter-fed AC electric machinery

That´s all, folks !

Thank you for your attention!

